

# Transmission Lines-2

**Dr. Naeem Ahmad Jan**

# REFLECTION COEFFICIENT

$$V(x,t) = V^+ e^{-\gamma x} + V^- e^{+\gamma x}$$

$$I(x,t) = I^+ e^{-\gamma x} + I^- e^{+\gamma x}$$

$$Z_0 = \frac{V^+}{I^+} \quad \Bigg| \quad -Z_0 = \frac{V^-}{I^-}$$

$$I(x,t) = \frac{V^+}{Z_0} e^{-\gamma x} - \frac{V^-}{Z_0} e^{+\gamma x}$$



# REFLECTION COEFFICIENT


$$V(x,t) = V^+ e^{-\gamma x} + V^- e^{+\gamma x}$$

$$I(x,t) = I^+ e^{-\gamma x} + I^- e^{+\gamma x}$$

$$Z_L = \frac{1+\Gamma}{1-\Gamma} \times Z_0$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\tau = \frac{2Z_L}{Z_L + Z_0}$$

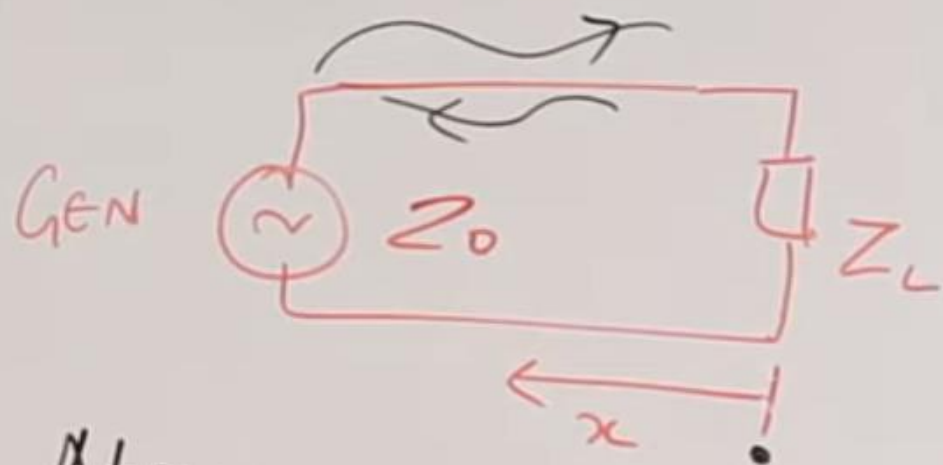

At  $x=0$

$$Z_L = \frac{V}{I} = \frac{V^+ + V^-}{V^+ - V^-} \times Z_0$$

$$Z_L = \frac{V^+ \left\{ 1 + \frac{V^-}{V^+} \right\}}{V^+ \left\{ 1 - \frac{V^-}{V^+} \right\}} \times Z_0$$


$$Z_L = \frac{1+\Gamma}{1-\Gamma} Z_0$$

$\Gamma = \frac{V^-}{V^+}$   
Reflection Coeff.
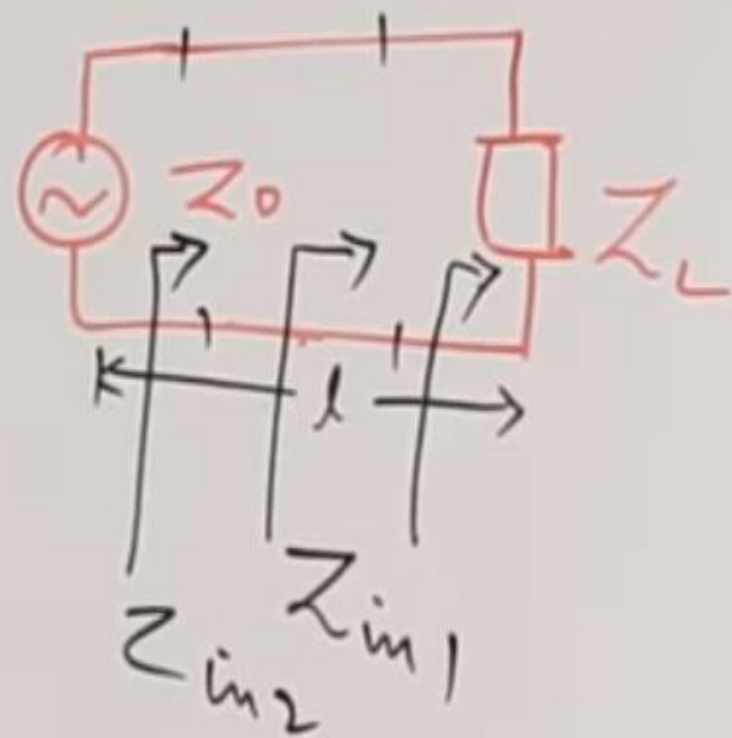
# INPUT IMPEDANCE OF TRANSMISSION LINE

① LOSSLESS MEDIUM.


$$Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$


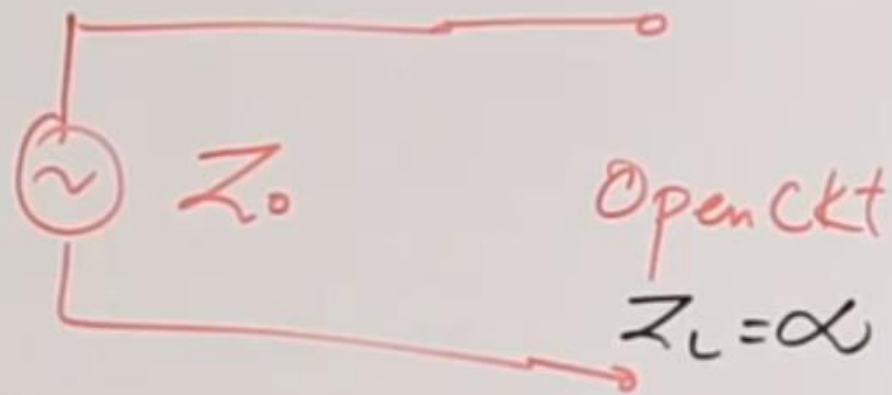
# INPUT IMPEDANCE OF OPEN CKT

$$Z_{in} = Z_0 \left\{ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right\}$$

$$Z_{in} = Z_0 \times \cancel{Z_L} \left\{ \frac{1 + j \frac{\cancel{Z_0}}{\cancel{Z_L}} \tan \beta l}{\cancel{Z_L} \left\{ \frac{\cancel{Z_0}}{\cancel{Z_L}} + j \tan \beta l \right\}} \right\}$$
$$= \frac{Z_0}{j \tan \beta l}$$




$$Z_{in} = -j Z_0 \cot \beta l$$

# INPUT IMPEDANCE OF SHORT CKT

$$Z_{in} = Z_0 \left\{ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right\}$$

$$Z_{in} = \cancel{Z_0} \left\{ \frac{0 + jZ_0 \tan \beta l}{\cancel{Z_0} + 0} \right\}$$

$$Z_{in} = jZ_0 \tan \beta l$$

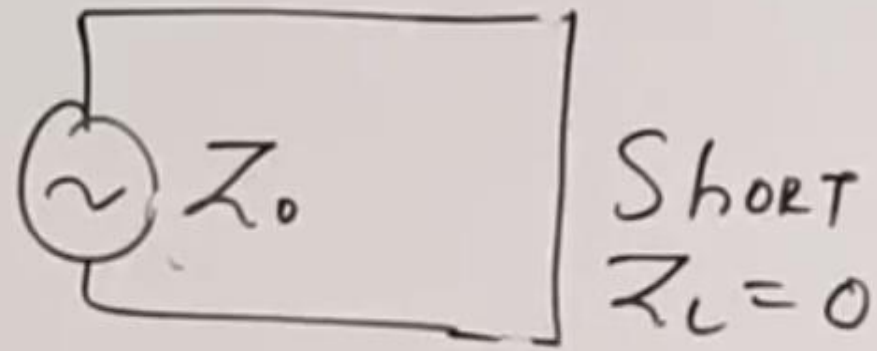


# INPUT IMPEDANCE OF $\lambda/4$ LENGTH OF TX LINE

$$Z_{in} = Z_0 \left\{ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right\}$$

$$Z_{in} = Z_0 \tan \beta l \left\{ \frac{Z_L \rightarrow 0}{\tan \beta l} + jZ_0 \right\}$$

$$\tan \beta l \left\{ \frac{Z_0 \rightarrow 0}{\tan \beta l} + jZ_L \right\}$$
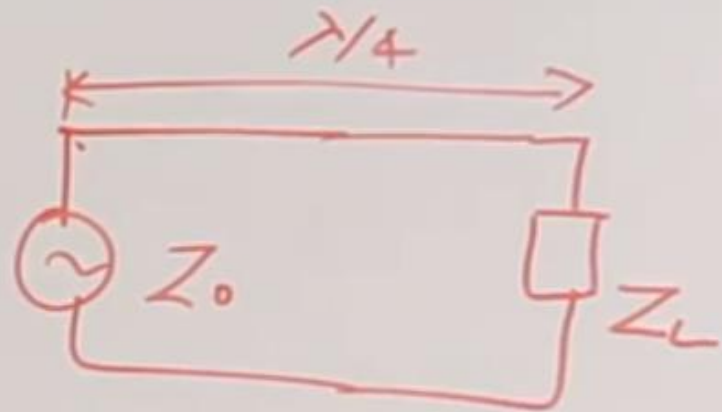
$$Z_{in} = Z_0 \times \frac{jZ_0}{jZ_L} = \frac{Z_0^2}{Z_L}$$



$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4}$$

$$= \frac{\pi}{2}$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

# POWER IN TRANSMISSION LINE

$$V(x,t) = (V^+ e^{-\gamma x} + V^- e^{+\gamma x}) e^{j\omega t}$$

FOR FORWARD PART

$$V(x,t) = V^+ e^{-\gamma x} e^{j\omega t}$$

$$\gamma = \alpha + j\beta$$

$$V(x,t) = V^+ e^{-(\alpha + j\beta)x} e^{j\omega t}$$

$$= V^+ e^{-\alpha x} e^{-j\beta x} e^{j\omega t}$$

$$= V^+ e^{-\alpha x} e^{+j(\omega t - \beta x)}$$

$$= V^+ e^{-\alpha x} \cos(\omega t - \beta x)$$

$$I(x,t) = I^+ e^{-\gamma x} + I^- e^{+\gamma x}$$

FOR FORWARD PART

$$I(x,t) = I^+ e^{-\alpha x} \cos(\omega t - \beta x)$$

$$P(x,t) = V(x,t) I(x,t)$$



# POWER IN TRANSMISSION LINE

$$P(x,t) = V^+ e^{-\alpha x} \cos(\omega t - \beta x) I^+ e^{-\alpha x} \cos(\omega t - \beta x + \theta)$$

$$P(x,t) = V^+ I^+ e^{-2\alpha x} \cos(\omega t - \beta x) \cos(\omega t - \beta x + \theta)$$

$$P_{av} = \frac{1}{T} \int_0^T P(x,t) dt$$

$$= \frac{1}{T} \int_0^T V^+ I^+ e^{-2\alpha x} \cos(\omega t - \beta x) \cos(\omega t - \beta x + \theta) dt$$

$$= V^+ I^+ e^{-2\alpha x} \cdot \frac{1}{T} \int_0^T \cos(\omega t - \beta x) \cos(\omega t - \beta x + \theta) dt$$

# POWER IN TRANSMISSION LINE

$$P = V^+ I^+ e^{-2\alpha x} \frac{1}{T} \int_0^T \left( \frac{1}{2} \cos(2\omega t - 2\beta x + \theta) + \frac{1}{2} \cos(\theta) \right) dt$$

$$= V^+ I^+ e^{-2\alpha x} \cdot \frac{1}{2} \cos \theta \cdot \frac{1}{T} \int_0^T dt$$

$$P = \frac{1}{2} V^+ I^+ e^{-2\alpha x} \cos \theta$$

$$= \frac{1}{2} V^+ \cdot \frac{V^+}{Z_0} e^{-2\alpha x} \cos \theta$$

$$= \frac{|V^+|^2}{2 Z_0} e^{-2\alpha x} \cos \theta \text{ W}$$

$$Z_0 = \frac{V^+}{I^+}$$


$$I^+ = \frac{V^+}{Z_0}$$

$$P = \frac{E^2}{2\eta} e^{-2\alpha z} \cos \theta$$

# VSWR

Voltage Standing Wave Ratio

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

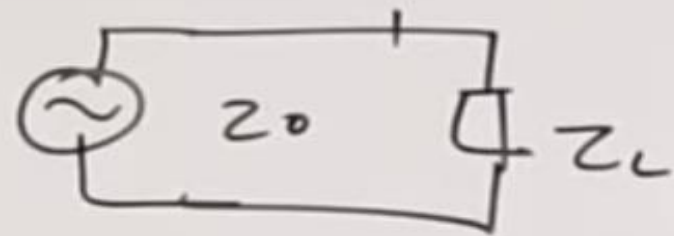

$$V_{max} \Leftrightarrow Z_{min} = \frac{-1}{2\beta} (\phi + (2m+1)\pi)$$

$$V_{min} \Leftrightarrow Z_{max} = \frac{-1}{2\beta} (\phi + 2m\pi)$$

$\left\{ \begin{array}{l} m = 0, 1, 2, \dots \end{array} \right.$




# VSWR (S)

Voltage Standing Wave Ratio

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Relation b/w V & I

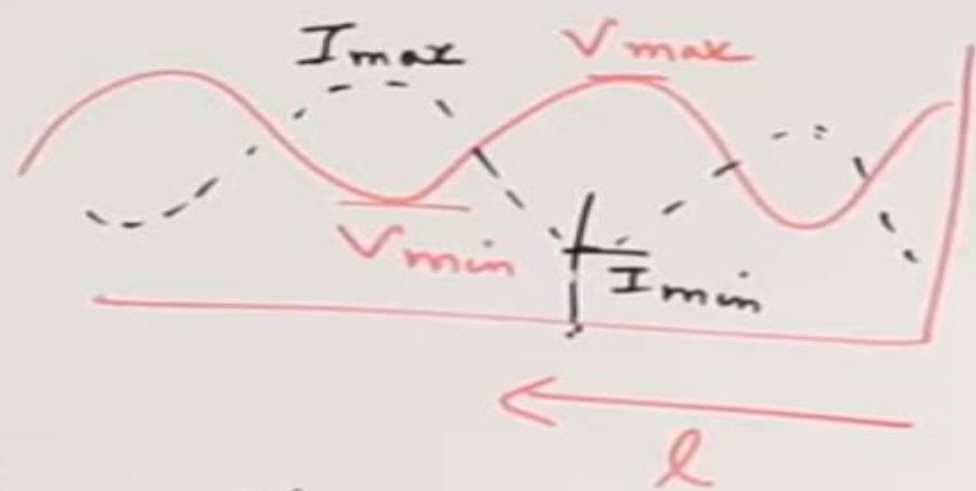

$$Z_{max} = \frac{V_{max}}{I_{min}} = Z_0 S$$

$$Z_{min} = \frac{V_{min}}{I_{max}} = \frac{Z_0}{S}$$

In the circuit shown all the transmission line sections are lossless.

The Voltage Standing Wave Ratio (VSWR) on the  $60\ \Omega$  line.


$$Z_a = \frac{Z_0^2}{Z_L} = \frac{(30\sqrt{2})^2}{30} = 60\ \Omega$$

$$Z_b = j Z_0 \tan \beta l = j 30 \tan \beta l$$

$$= j 30 \tan \frac{2\pi}{8} \cdot \frac{\lambda}{8}$$


$$= j 30 \tan \frac{\pi}{4}$$

$$= +j 30$$

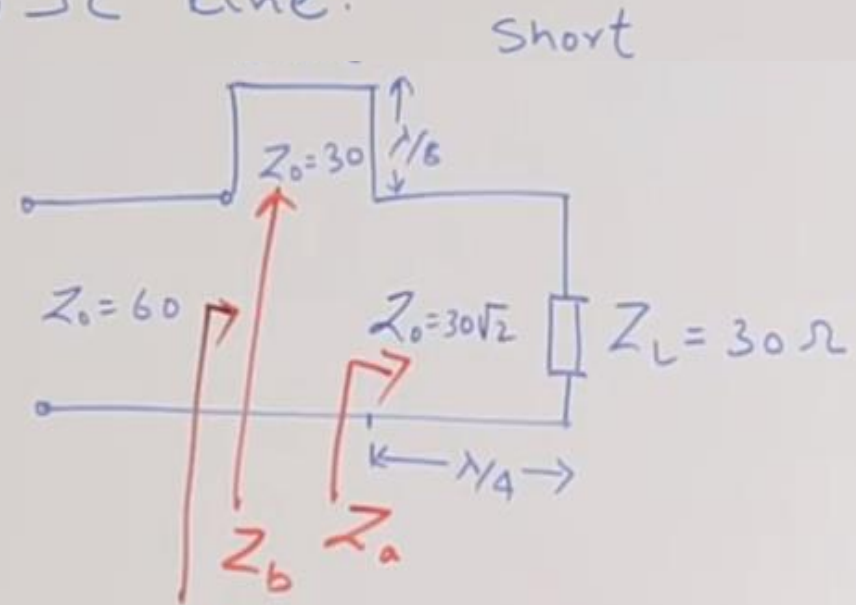

$$Z_{eqL} = Z_a + Z_b$$

$$Z_{eqL} = 60 + 30j$$

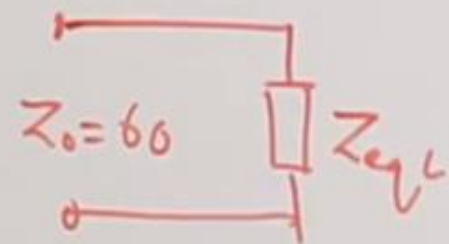


circuit shown all the transmission line section are lossless.  
 Standing Wave Ratio (VSWR) on the  $60\ \Omega$  line.

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$


$$\Gamma = \frac{Z_{eqL} - Z_0}{Z_{eqL} + Z_0} = \frac{60 + 30j - 60}{60 + 30j + 60}$$

$$\Gamma = \frac{30j}{120 + 30j}, \quad |\Gamma| = 0.24$$

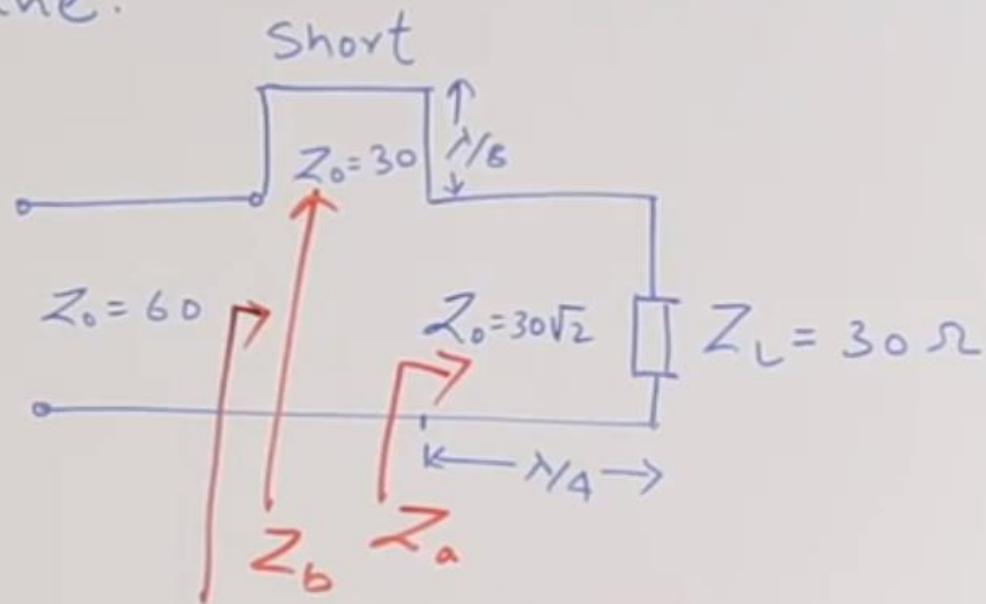

$$Z_{eqL} = Z_a + Z_b$$


$$Z_{eqL} = 60 + 30j$$

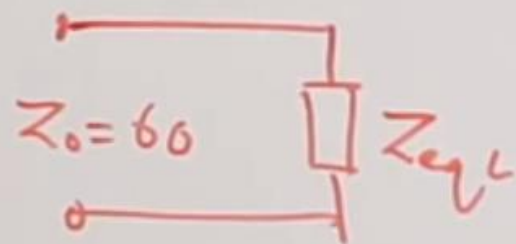

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$= \frac{1 + 0.2425}{1 - 0.2425}$$

$$VSWR = 1.64$$

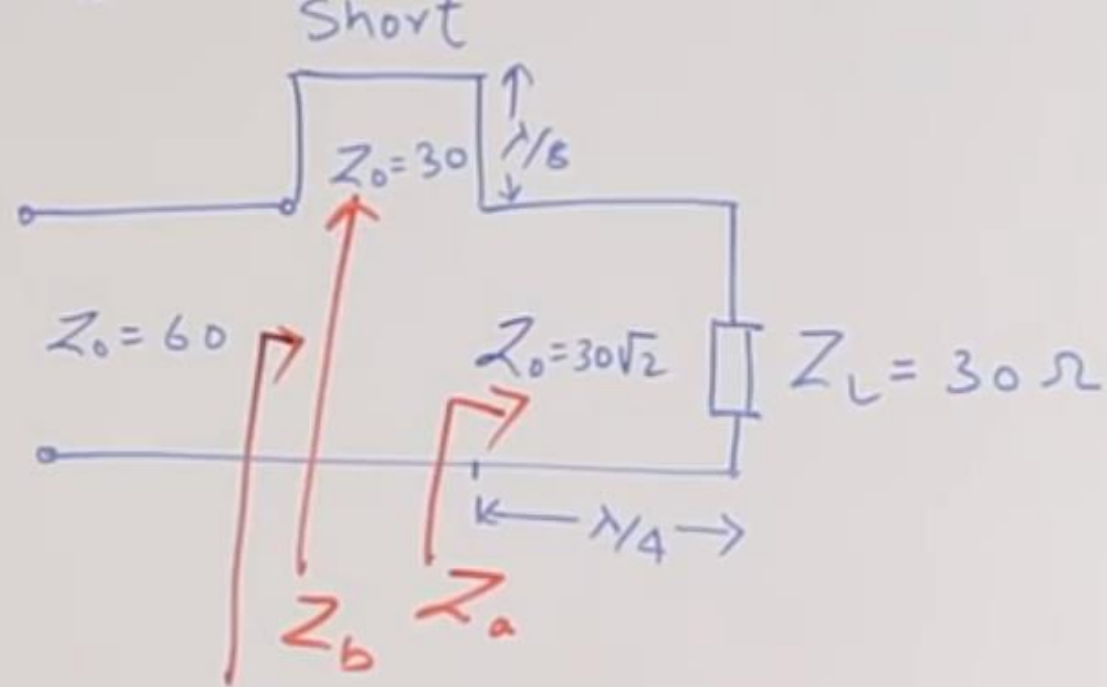

$$Z_{eqL} = Z_a + Z_b$$

$$Z_{eqL} = 60 + 30j$$

