

### SECTION 2-1 CHECKUP

Answers can be found at  
www.pearsonhighered.com/  
floyd.

1. Describe forward bias of a diode.
2. Explain how to forward-bias a diode.
3. Describe reverse bias of a diode.
4. Explain how to reverse-bias a diode.
5. Compare the depletion regions in forward bias and reverse bias.
6. Which bias condition produces majority carrier current?
7. How is reverse current in a diode produced?
8. When does reverse breakdown occur in a diode?
9. Define *avalanche effect* as applied to diodes.

## 2-2 VOLTAGE-CURRENT CHARACTERISTIC OF A DIODE

As you have learned, forward bias produces current through a diode and reverse bias essentially prevents current, except for a negligible reverse current. Reverse bias prevents current as long as the reverse-bias voltage does not equal or exceed the breakdown voltage of the junction. In this section, we will examine the relationship between the voltage and the current in a diode on a graphical basis.

After completing this section, you should be able to

- **Analyze the voltage-current ( $V$ - $I$ ) characteristic of a diode**
- Explain the  $V$ - $I$  characteristic for forward bias
  - ♦ Graph the  $V$ - $I$  curve for forward bias
  - ♦ Describe how the barrier potential affects the  $V$ - $I$  curve
  - ♦ Define *dynamic resistance*
- Explain the  $V$ - $I$  characteristic for reverse bias
  - ♦ Graph the  $V$ - $I$  curve for reverse bias
- Discuss the complete  $V$ - $I$  characteristic curve
  - ♦ Describe the effects of temperature on the diode characteristic


### $V$ - $I$ Characteristic for Forward Bias

When a forward-bias voltage is applied across a diode, there is current. This current is called the *forward current* and is designated  $I_F$ . Figure 2-9 illustrates what happens as the forward-bias voltage is increased positively from 0 V. The resistor is used to limit the forward current to a value that will not overheat the diode and cause damage.

With 0 V across the diode, there is no forward current. As you gradually increase the forward-bias voltage, the forward current *and* the voltage across the diode gradually increase, as shown in Figure 2-9(a). A portion of the forward-bias voltage is dropped across the limiting resistor. When the forward-bias voltage is increased to a value where the voltage across the diode reaches approximately 0.7 V (barrier potential), the forward current begins to increase rapidly, as illustrated in Figure 2-9(b).


As you continue to increase the forward-bias voltage, the current continues to increase very rapidly, but the voltage across the diode increases only gradually above 0.7 V. This small increase in the diode voltage above the barrier potential is due to the voltage drop across the internal dynamic resistance of the semiconductive material.

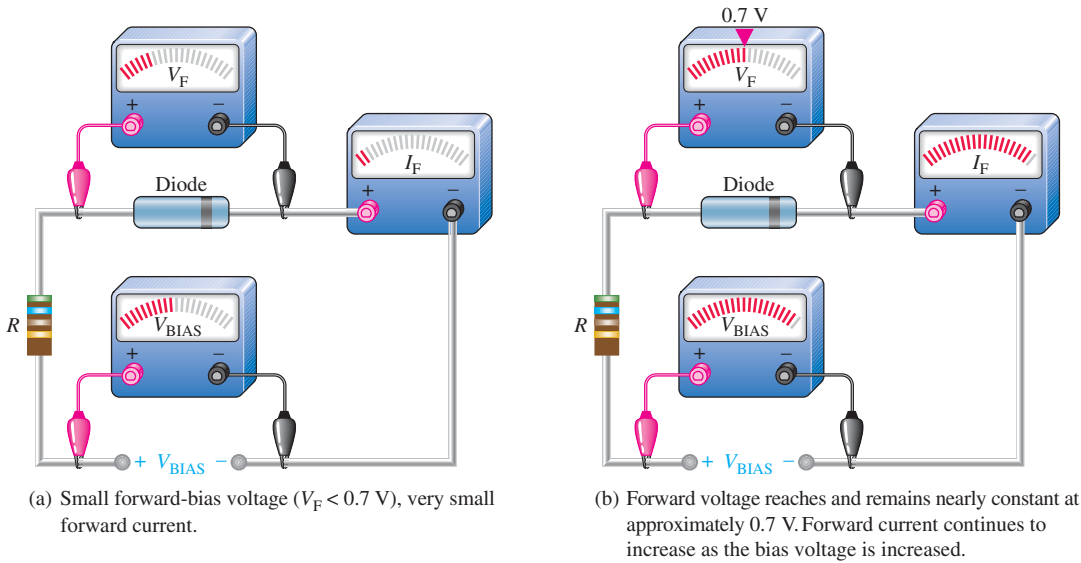**Graphing the  $V$ - $I$  Curve** If you plot the results of the type of measurements shown in Figure 2-9 on a graph, you get the  **$V$ - $I$  characteristic** curve for a forward-biased diode, as shown in Figure 2-10(a). The diode forward voltage ( $V_F$ ) increases to the right along the horizontal axis, and the forward current ( $I_F$ ) increases upward along the vertical axis.




▲ FIGURE 2-9

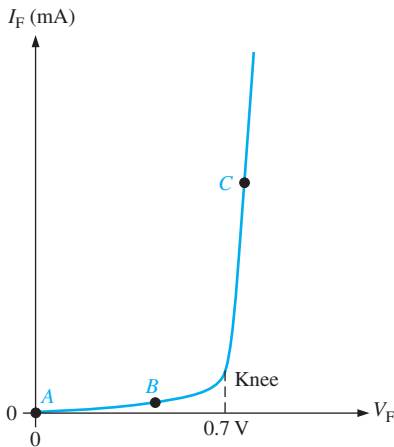Forward-bias measurements show general changes in  $V_F$  and  $I_F$  as  $V_{BIAS}$  is increased.



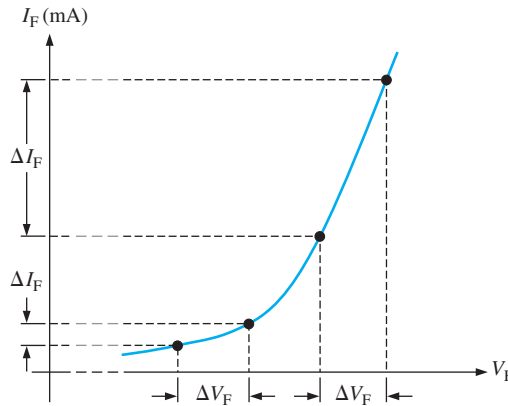(a)  $V$ - $I$  characteristic curve for forward bias.



(b) Expanded view of a portion of the curve in part (a). The dynamic resistance  $r'_d$  decreases as you move up the curve, as indicated by the decrease in the value of  $\Delta V_F / \Delta I_F$ .

◀ FIGURE 2-10

Relationship of voltage and current in a forward-biased diode.

As you can see in Figure 2-10(a), the forward current increases very little until the forward voltage across the  $pn$  junction reaches approximately  $0.7\text{ V}$  at the knee of the curve. After this point, the forward voltage remains nearly constant at approximately  $0.7\text{ V}$ , but  $I_F$  increases rapidly. As previously mentioned, there is a slight increase in  $V_F$  above  $0.7\text{ V}$  as the current increases due mainly to the voltage drop across the dynamic resistance. The  $I_F$  scale is typically in mA, as indicated.

Three points A, B, and C are shown on the curve in Figure 2-10(a). Point A corresponds to a zero-bias condition. Point B corresponds to Figure 2-10(a) where the forward voltage is less than the barrier potential of  $0.7\text{ V}$ . Point C corresponds to Figure 2-10(a) where the forward voltage *approximately* equals the barrier potential. As the external bias voltage and forward current continue to increase above the knee, the forward voltage will increase slightly above  $0.7\text{ V}$ . In reality, the forward voltage can be as much as approximately  $1\text{ V}$ , depending on the forward current.

**Dynamic Resistance** Figure 2–10(b) is an expanded view of the  $V$ - $I$  characteristic curve in part (a) and illustrates dynamic resistance. Unlike a linear resistance, the resistance of the forward-biased diode is not constant over the entire curve. Because the resistance changes as you move along the  $V$ - $I$  curve, it is called *dynamic* or *ac resistance*. Internal resistances of electronic devices are usually designated by lowercase italic  $r$  with a prime, instead of the standard  $R$ . The dynamic resistance of a diode is designated  $r'_d$ .

Below the knee of the curve the resistance is greatest because the current increases very little for a given change in voltage ( $r'_d = \Delta V_F / \Delta I_F$ ). The resistance begins to decrease in the region of the knee of the curve and becomes smallest above the knee where there is a large change in current for a given change in voltage.


### $V$ - $I$ Characteristic for Reverse Bias

When a reverse-bias voltage is applied across a diode, there is only an extremely small reverse current ( $I_R$ ) through the  $pn$  junction. With 0 V across the diode, there is no reverse current. As you gradually increase the reverse-bias voltage, there is a very small reverse current and the voltage across the diode increases. When the applied bias voltage is increased to a value where the reverse voltage across the diode ( $V_R$ ) reaches the breakdown value ( $V_{BR}$ ), the reverse current begins to increase rapidly.

As you continue to increase the bias voltage, the current continues to increase very rapidly, but the voltage across the diode increases very little above  $V_{BR}$ . Breakdown, with exceptions, is not a normal mode of operation for most  $pn$  junction devices.

**Graphing the  $V$ - $I$  Curve** If you plot the results of reverse-bias measurements on a graph, you get the  $V$ - $I$  characteristic curve for a reverse-biased diode. A typical curve is shown in Figure 2–11. The diode reverse voltage ( $V_R$ ) increases to the left along the horizontal axis, and the reverse current ( $I_R$ ) increases downward along the vertical axis.

There is very little reverse current (usually  $\mu A$  or  $nA$ ) until the reverse voltage across the diode reaches approximately the breakdown value ( $V_{BR}$ ) at the knee of the curve. After this point, the reverse voltage remains at approximately  $V_{BR}$ , but  $I_R$  increases very rapidly, resulting in overheating and possible damage if current is not limited to a safe level. The breakdown voltage for a diode depends on the doping level, which the manufacturer sets, depending on the type of diode. A typical rectifier diode (the most widely used type) has a breakdown voltage of greater than 50 V. Some specialized diodes have a breakdown voltage that is only 5 V.

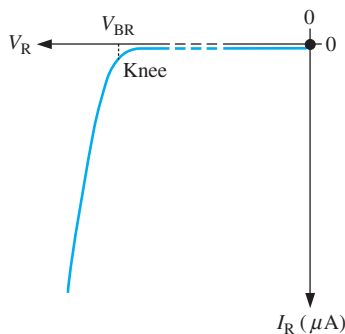

▲ FIGURE 2–11


$V$ - $I$  characteristic curve for a reverse-biased diode.

### The Complete $V$ - $I$ Characteristic Curve


Combine the curves for both forward bias and reverse bias, and you have the complete  $V$ - $I$  characteristic curve for a diode, as shown in Figure 2–12.

► FIGURE 2–12

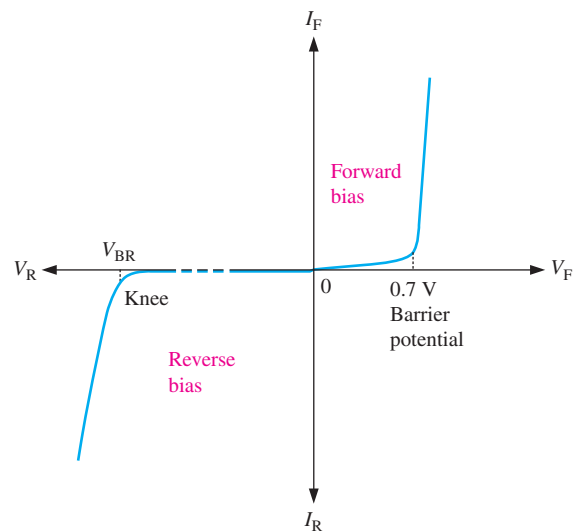The complete  $V$ - $I$  characteristic curve for a diode.



**Temperature Effects** For a forward-biased diode, as temperature is increased, the forward current increases for a given value of forward voltage. Also, for a given value of forward current, the forward voltage decreases. This is shown with the  $V$ - $I$  characteristic curves in Figure 2–13. The blue curve is at room temperature ( $25^{\circ}\text{C}$ ) and the red curve is at an elevated temperature ( $25^{\circ}\text{C} + \Delta T$ ). The barrier potential decreases by 2 mV for each degree increase in temperature.

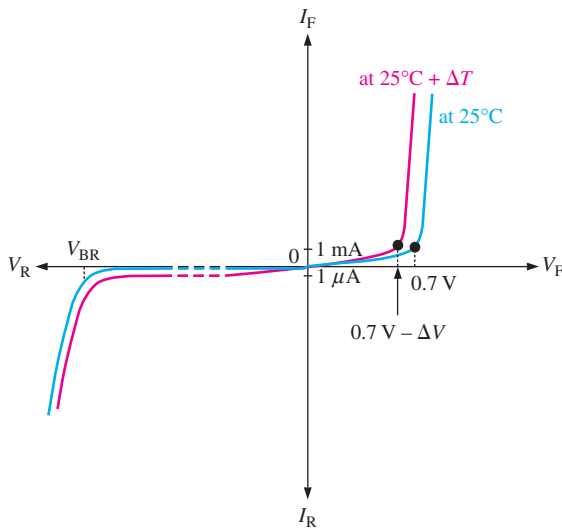

◀ **FIGURE 2–13**

Temperature effect on the diode  $V$ - $I$  characteristic. The 1 mA and 1  $\mu\text{A}$  marks on the vertical axis are given as a basis for a relative comparison of the current scales.

For a reverse-biased diode, as temperature is increased, the reverse current increases. The difference in the two curves is exaggerated on the graph in Figure 2–13 for illustration. Keep in mind that the reverse current below breakdown remains extremely small and can usually be neglected.

#### SECTION 2–2 CHECKUP

1. Discuss the significance of the knee of the characteristic curve in forward bias.
2. On what part of the curve is a forward-biased diode normally operated?
3. Which is greater, the breakdown voltage or the barrier potential?
4. On what part of the curve is a reverse-biased diode normally operated?
5. What happens to the barrier potential when the temperature increases?

## 2–3 DIODE MODELS

You have learned that a diode is a  $pn$  junction device. In this section, you will learn the electrical symbol for a diode and how a diode can be modeled for circuit analysis using any one of three levels of complexity. Also, diode packaging and terminal identification are introduced.

After completing this section, you should be able to

- **Explain how the three diode models differ**
- Discuss bias connections
- Describe the diode approximations
  - ♦ Describe the ideal diode model
  - ♦ Describe the practical diode model
  - ♦ Describe the complete diode model