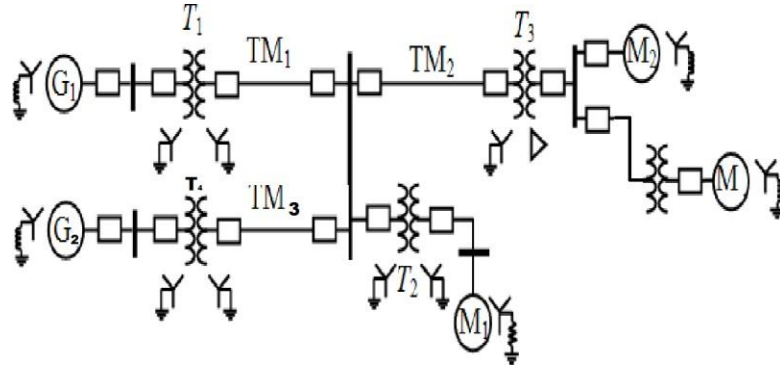


Power System Analysis


Assignment

Total Marks=20

1. Prepare an Impedance diagram and a Reactance diagram from the single line diagram shown in figure.



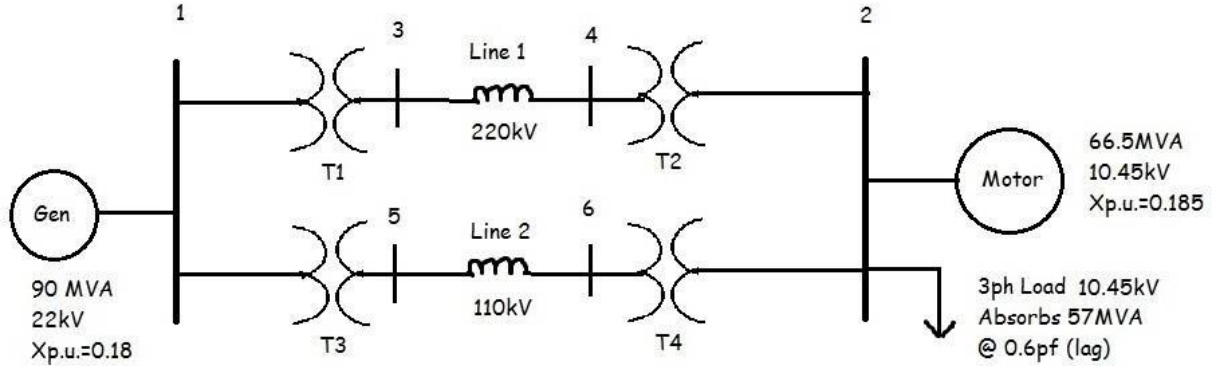
2. A transformer is rated 20kV/200kV, 350MVA and has an internal impedance of $j6.4\Omega$ as seen from the low voltage side. Consider 22kV, 400 MVA as base and show that V_{pu} , S_{pu} and Z_{pu} is same for the both sides of this transformer.
3. Find per unit impedances for the following figure.




T1:	50MVA	22/220kV	$X_{p.u.} = 0.10$
T2:	40MVA	220/11kV	$X_{p.u.} = 0.06$
T3:	40MVA	22/110kV	$X_{p.u.} = 0.064$
T4:	40MVA	110/11kV	$X_{p.u.} = 0.08$
Line 1:	48.4 Ohms (total)		
Line 2:	65.43 Ohms (total)		


PEguru.com

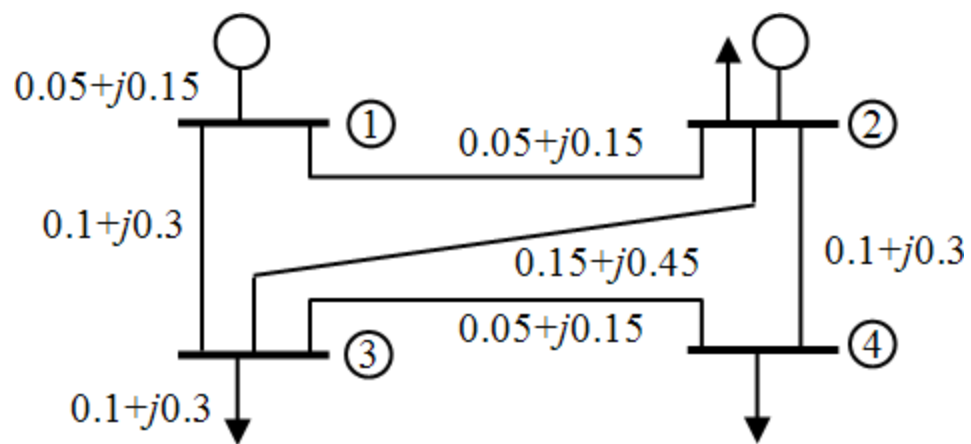4. Make the admittance matrix, Y_{bus} , for the following network. Given parameters are impedance in per-unit.



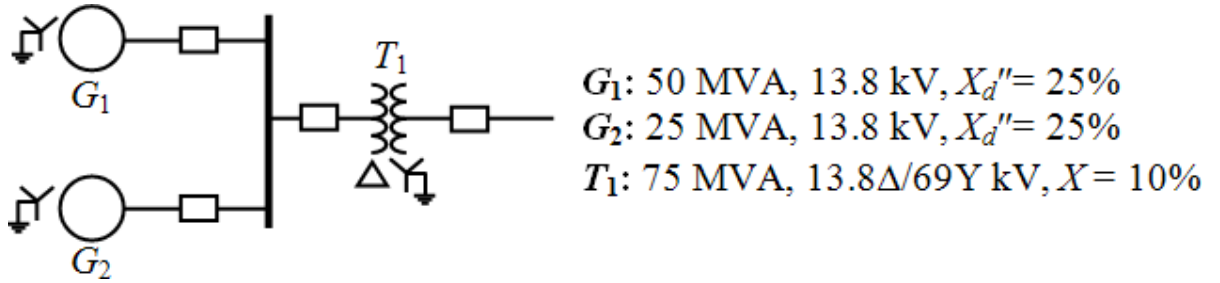

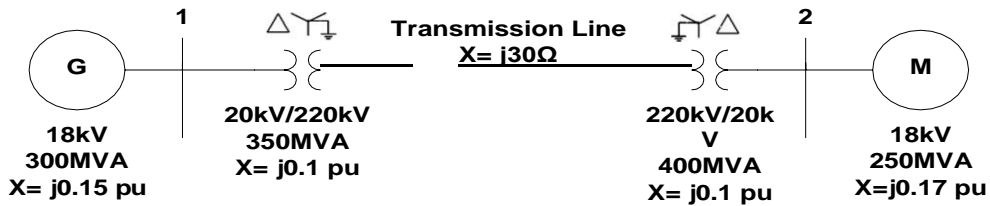5. In the figure 11 the motor is drawing 200MW at 0.8 power factor lagging at a terminal voltage of 17.8kV, when a bolted three phase short circuit occurs at bus 2. Consider the rating of generator G, as base at generator circuit for per unit calculation of the system and find total sub-transient fault current and sub-transient generator and motor current in per unit neglecting pre-fault current.



6. What will be the sub-transient generator and motor current in per unit if pre-fault current is considered?