

Department of Electrical Engineering
Sessional Assignment
Course Details

Course Title: Electric Power Distribution & Utilization **Module:** 3rd (BTech)

Student Details

Name: _____ **Student ID:** _____

Q1: A 2-wire D.C. distributor AB is fed from both ends. At feeding point A, the voltage is maintained as at A 240 V and at B 250 V. The total length of the distributor is 300 meters and loads are tapped off as under:

25 A at 50 meters from A; 50 A at 75 meters from A

30 A at 100 meters from A; 40 A at 150 meters from A

The resistance per kilometer of one conductor is 0.5Ω . Calculate:

- (i) Currents in various sections of the distributor
 - (ii) Minimum voltage and the point at which it occurs
-

Q2: A 2-wire D.C. distributor cable AB is 1 km long and supplies loads of 100A, 150A, 200A and 50A situated 500 m, 1000 m, 1500 m and 1000 m from the feeding point A. Each conductor has a resistance of 0.02Ω per 1000 m. Calculate the p.d. at each load point if a p.d. of 400 V is maintained at point A.