

Chapter #4 :- "BIPOLAR JUNCTION TRANSISTORS (BJT)"



⇒ BJT :-

- \* <sup>transistor was</sup> invented in Dec 1947 at bell labs at USA.
- \* BJT is a three terminal device and it is used in amplification of weak signals and used in switching operation.

→ Physical Structure:



INPN

IPNP

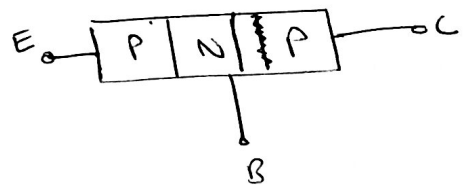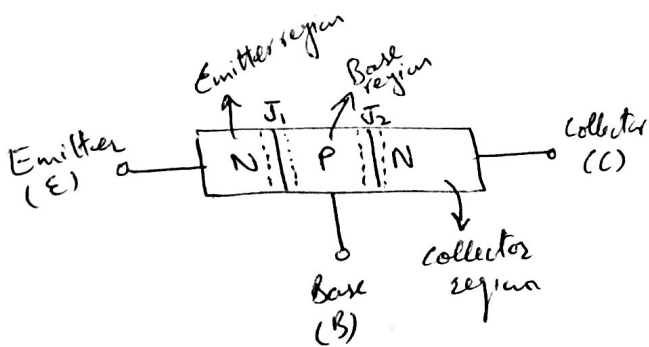



- \* 2 junctions (N)
- \* 1 " (P)
- \*  $J_1 \rightarrow$  emitter-base
- \*  $J_2 \rightarrow$  collector-base
- \* There is depletion region at  $J_1$
- \* There is depletion region at  $J_2$

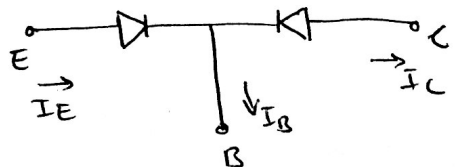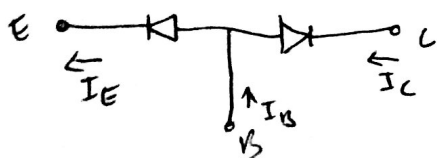widths:  $C > E > B$   
doping:  $E > C > B$




→ Cross-section View:-

**NPN**

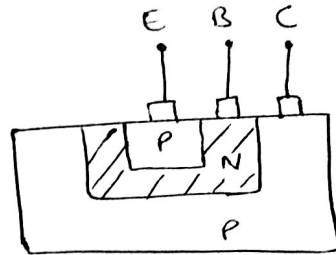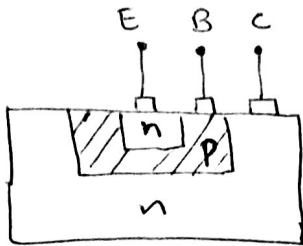


→ Symbol:

**NPN**

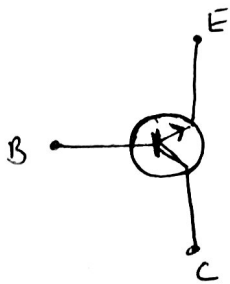

\* in case of NPN the  $e^-$  will move from B  $\rightarrow$  E

**PNP**

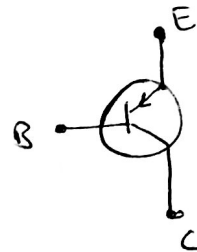

\* in case of PNP the  $e^-$  will move from E  $\rightarrow$  B

# Why Bipolar Junction Transistor?

- \* Bipolar:  $e^-$  and holes.
- \* Junction:  $J_1$  and  $J_2$
- \* Transistor: Transfer + resistor.

$J_1 \rightarrow$  F.B : will offer low resistance } active mod.

$J_2 \rightarrow$  R.B : " " high " }


So, BJT transfer a signal from low to high resistance.

## Regions of Operation:

$J_1$	$J_2$	Region of operation	
F.B	R.B	Active	Amplifier.
F.B	F.B	Saturation	"ON" switch
R.B	R.B	Cut off	"OFF" / open circuit
R.B	F.B	Inverted	rarely used.
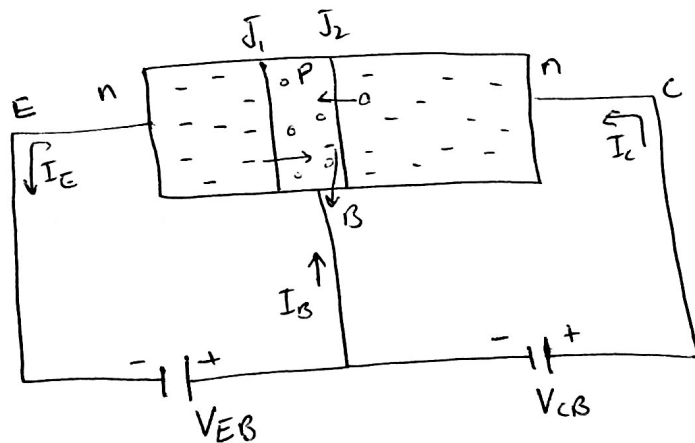
## Working of BJT:-

- \* This is an npn transistor.
- \* we operate it in Active Mode.



\* Here in active mode we have  $J_1 =$  F.B and  $J_2 =$  R.B


~~also~~

→ Analyze Movement of  $e^-$  :-

\* Let's say  $V_b$  is barrier potential for  $J_1$  and  $J_2$ .

$$V_b \rightarrow J_1, J_2$$

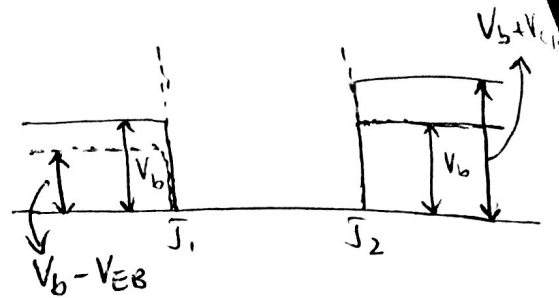\* After application of  $V_{BE}$ , the junction  $J_1$  is F.B, so the barrier potential will now reduce and new barrier potential will be  $V_b - V_{BE}$



\* After application of  $V_{CB}$ , the  $J_2$  is R.B, so the B.P will increase and new B.P will be  $V_b + V_{CB}$

\* Because of reduce B.P at  $J_1$ , the  $e^-$  will move into P-region and recombine with holes at Base. We know that base is very small and lightly doped. So the recombination of  $e^-$  and holes is very small and most of  $e^-$  pass over into n-region at 'C'. (95% - 98%).

\* very few  $e^-$  recombine with hole and will move into Base ( $V_{EB}$ ). (2% - 5%)

\*  $J_2$  is R.B so there must be a reverse saturation current ( $I_{CO}$ ) or leakage current due to minority carriers in N and P regions.

$I_{CO}$ : c: collector  
o: open circuit. we measure it when  $V_{EB}$  is open circuit.

\* If we find  $I_c$ .

$$I_c = \alpha I_E + I_{CO}$$

\* Next we find relationship b/w  $I_E$ ,  $I_B$  and  $I_C$ .  
first we see direction of current: e.

Use KCL:


Sum of current entering = Sum of current leaving.

$$I_c + I_B = I_E$$

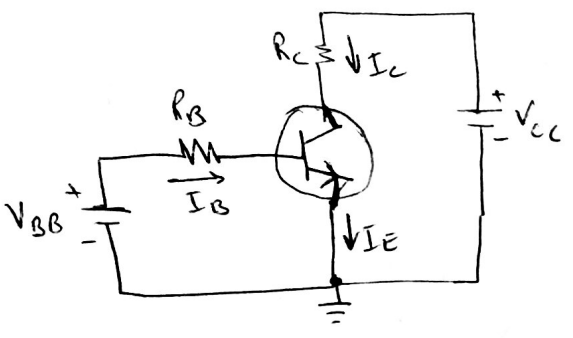
# Transistor Characteristics & Curves:

\* When a transistor is connected to DC bias voltages, for both npn and PNP types.

- \*  $V_{BB}$  F.B the base-emitter junction.
- \*  $V_{CC}$  R.B " " - collector "



(a) NPN

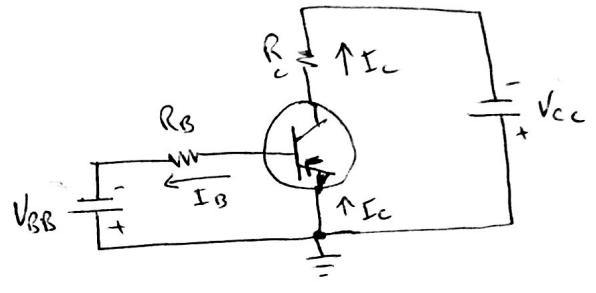

(b) PNP

\* From above (a) and (b) we can see that current  $I_E$  is sum of  $I_C$  and  $I_B$ .

## DC beta and DC alpha: $\beta_{DC}$ , $\alpha_{DC}$

\* \* The DC current gain of a transistor is the ratio of the DC collector current ( $I_C$ ) to the DC base current ( $I_B$ ) and is designated as DC beta current.

$$\beta_{DC} = \frac{I_C}{I_B}$$

\*  $\beta_{DC}$  ranges from 20 - 200 or higher. Sometimes the  $\beta_{DC}$  is called equivalent hybrid (h) parameter  $h_{FE}$  i.e.

$$h_{FE} = \beta_{DC}$$

\* \* The ratio of the DC collector current ( $I_C$ ) to the DC emitter current ( $I_E$ ) is the alpha DC ( $\alpha_{DC}$ ):

$$\alpha_{DC} = \frac{I_C}{I_E}$$

- \*  $\alpha_{DC}$  is less used as compared to  $\beta_{DC}$
- \*  $\alpha_{DC}$  ranges from 0.95 to 0.99 or higher, but is always less than 1.

Exp 4.1:- Find  $\beta_{DC} = ?$ ,  $I_E = ?$ ,  $I_B = 50 \mu A$ ,  $I_C = ?$

Soln.  $\beta_{DC} = I_C / I_B = \frac{3.65 \text{ mA}}{50 \mu A} = 73.$


and  $I_E = I_B + I_C = 50 \mu A + 3.65 \text{ mA} = 3.75 \text{ mA}.$

### ⇒ BJT Circuit Analysis :-

\* Consider the basic transistor bias circuit configuration in figure below

\* Three transistor DC currents and three DC voltages can be identified:

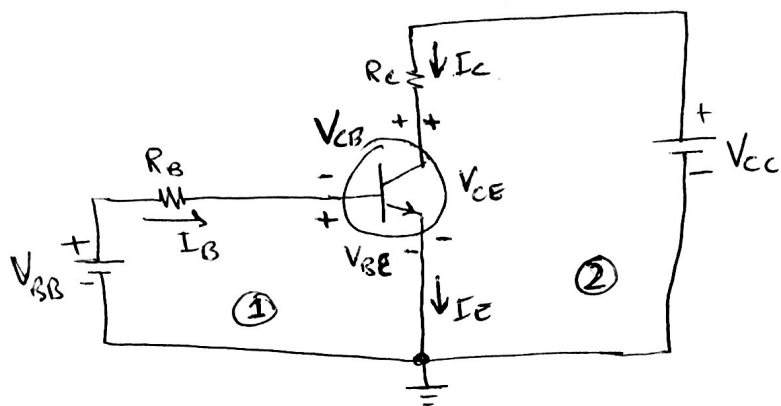- $I_B$ : DC base current
- $I_E$ : DC emitter "
- $I_C$ : " collector "
- $V_{BE}$ : DC volt. at base w.r.t emitter
- $V_{CB}$ : DC volt. at collector w.r.t base
- $V_{CE}$ : DC volt. at collector w.r.t emitter.



"Transistor currents & voltages"

\*  $V_{BB}$  forward biases the base-emitter junction, and the  $V_{CC}$  reverse " " " - collector " .

\* When base-emitter junction is F.B, it is like a F.B diode and has a nominal forward voltage drop of :  $V_{BE} = 0.7 \text{ V}.$

\* Since emitter is at ground (0V), apply KVL<sup>①</sup> to solve for  $V_{RB}$ .

$$V_{RB} = V_{BB} - V_{BE}$$

using ohm's law :  $V_{RB} = I_B R_B.$

$$I_B R_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

\* Now the voltage at the collector w.r.t ground emitter is given by KVL at (2):

$$V_{CE} = V_{CC} - V_{Rc}$$

also,  $V_{Rc} = I_c R_c$

$$\boxed{V_{CE} = V_{CC} - I_c R_c}$$

where,  $I_c = I_B \beta_{DC}$

\* To solve for volt. across the reverse biased collector-base junction is.


$$V_{CE} = V_{CB} + V_{BE}$$

$$\boxed{V_{CB} = V_{CE} - V_{BE}}$$

Exp. 4.2 :- Find  $I_c, I_B, I_E, V_{BC}, V_{CE}, V_{CB}$ .  $\beta_{DC} = 150$ .

Sol:

$$V_{BE} \approx 0.7V$$

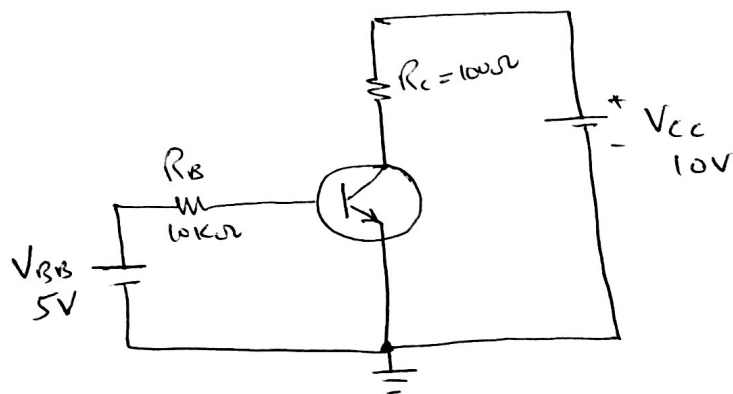

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{10k\Omega} = 430\mu A$$

$$I_c = \beta_{DC} I_B = (150)(430\mu A) = 64.5mA$$

$$I_E = I_c + I_B = 64.5mA + 430\mu A = 64.9mA$$

Now we solve for  $V_{CE}$  and  $V_{CB}$ .

$$V_{CE} = V_{CC} - I_c R_c = 10V - (64.5mA)(100\Omega) = 10V - 6.45V = 3.55V$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55V - 0.7V = 2.85V$$