

# Electronics 1

## Lecture #14

18/1/2018

- LED
- PD
- LASER
- PIN
- Shottky


→ Exercise Problems:-

- ①, ③, ④, ⑤, ⑥, ⑦, ⑧, ⑨, ⑩, ⑬, ⑰, ⑲, ⑳, ㉑, ㉒, ㉓, ㉔, ㉕, ㉖, ㉗, ㉘, ㉙.


P. 25:- Find R of PD?

①

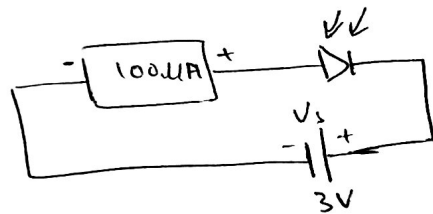
$$R = \frac{V_s}{I} = \frac{3V}{100\mu A} = 30k\Omega$$



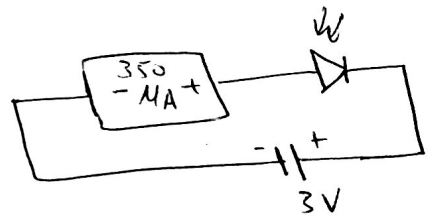②  $R = \frac{V_s}{I} = \frac{3V}{350\mu A} = 8.57k\Omega$



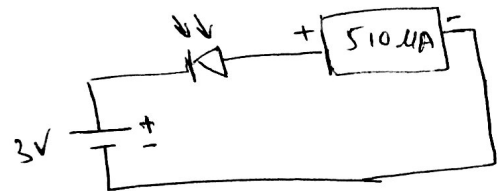③  $R = \frac{V_s}{I} = \frac{3V}{510\mu A} = 5.88k\Omega$



P. 26: The reading of micrometer will increase

P. 27: Varactor diode current change: 0.25mA to 0.15mA  
 when volt. " : 125mV to 200mV.  
 Find resistance R = ?

Sol

$$R = \frac{\Delta V}{\Delta I} = \frac{125mV - 200mV}{0.25 - 0.15mA} = \frac{-75mV}{0.10mA} = -750\Omega$$

3-10 From LED data sheet in Fig. 3-31 in Floyd 7th Ed. find?

(a) Radiant Intensity =  $I_e = ?$  at 900 nm

Max. output of LED = 15 mW/sr

from relative spectral emission graph in Fig. 3-31(c) the relative radiant intensity is approx. 0.75.

Therefore the  $I_e = 0.75 (15 \text{ mW/sr}) = 11.3 \text{ mW/sr}$ .

(b) Find forward voltage  $V_F$  drop = ? for  $I_F = 20 \text{ mA}$

From graph in part (c)  $V_F = 1.23 \text{ V}$  for  $I_F = 20 \text{ mA}$

(c) Radiant Intensity,  $I_e = ?$  at  $I_F = 30 \text{ mA}$

From graph in part (e)  $I_e = 5 \text{ mW/sr}$  for  $I_F = 30 \text{ mA}$ .

(d) max. Irradiance =  $H = ?$

distance =  $d = 10 \text{ cm}$ .


$$H = \frac{I_e}{d^2} = \frac{15 \text{ mW/sr}}{(10 \text{ cm})^2} = 0.15 \text{ mW/cm}^2$$

### Exercise Problems

3-11

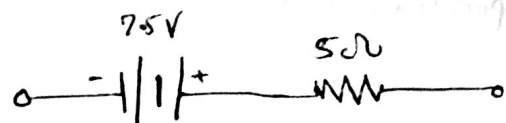(1) Zener diode has  $V_Z = 7.5 \text{ V}$   
 $Z_Z = 5 \Omega$  ] at certain current.

Draw equivalent circuit = ?  
of Zener diode



(2) ~~When reverse current is applied to~~  
reverse current in Zener diode increases from 20 mA to 30 mA  
the voltage " " changes " 5.6 V to 5.65 V.

Find Impedance  $Z_Z = ?$

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{5.65 - 5.6}{30 - 20} = \frac{0.05}{10} = 5 \Omega$$

(4) Given to students in Assignment #3.

(5) " " " " " "

Determine the min. input voltage? required for regulation to be established in fig.

Assume Ideal Zener diode


$$I_{zk} = 1.5 \text{ mA}$$

$$V_z = 14 \text{ V}$$

$$V_{in(\text{min})} = V_z + I_{zk} R$$

$$V_{in(\text{min})} = 14 \text{ V} + (1.5 \text{ mA})(560 \Omega)$$

$$V_{in(\text{min})} = 14.8 \text{ V}$$

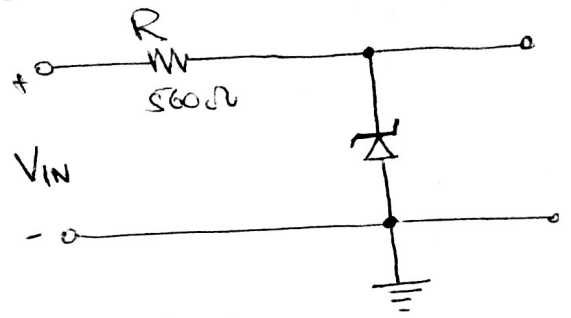

7 Assignment #3.

8\* Find  $R = ?$  at  $I_z = 40 \text{ mA}$

$$V_z = 12 \text{ V at } 30 \text{ mA, } Z_z = 30 \Omega$$

First we find,


$$\Delta V_z = I_z Z_z = (40 \text{ mA} - 30 \text{ mA})(30 \Omega)$$

$$\Delta V_z = 0.3 \text{ V}$$

From  $\Delta V_z$  above and  $V_z$  12V we will find  $V_z$  at 40mA as follows:

$$V_z = 12 \text{ V} + \Delta V_z = 12 \text{ V} + 0.3 \text{ V} = 12.3 \text{ V}$$
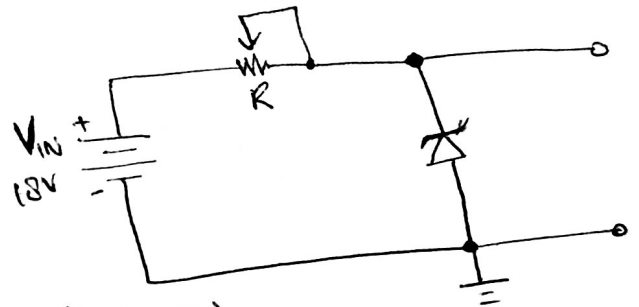
$$R = \frac{V_{in} - V_z}{40 \text{ mA}} = \frac{18 \text{ V} - 12.3 \text{ V}}{40 \text{ mA}} = 143 \Omega$$




9

Peak sinusoidal voltage is applied to above circuit. Draw output waveform. of P(8).

$$V_z = 12 \text{ V} + 0.3 \text{ V}$$

$$V_z = 12.3 \text{ V}$$

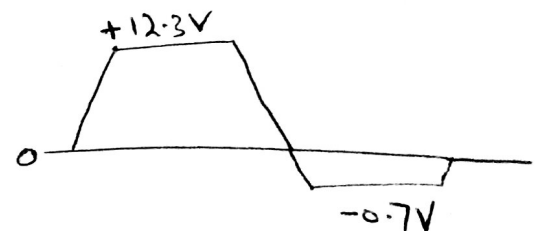


⑩ Assignment #3

⑬ Find capacitance value  $C=?$  to produce resonant freq. of  $1\text{MHz}$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{1}{4\pi^2 f^2 L}$$
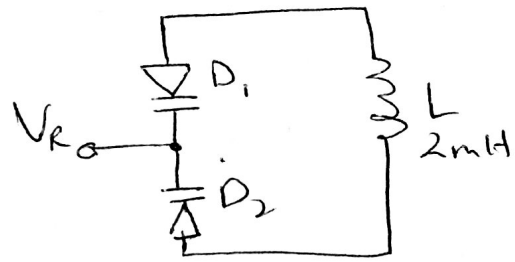
$$= \frac{1}{4\pi^2 (2\text{mH})(1\text{MHz})^2} = 12.7\text{pF}$$




\* Since both varactors are in series, so each should have a capacitance of  $2C_T = 25.4\text{pF}$ .

⑮ What is resistance of each photodiode in below fig.

$$R = \frac{V_s}{I} = \frac{3\text{V}}{510\mu\text{A}}$$

$$R = 5.88\text{k}\Omega$$

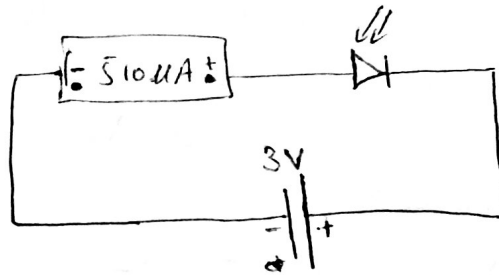

⑯ we assume  $V_f = 1.2\text{V}$ , Give  $V_s = 24\text{V}$ ,  $R = 680\Omega$ , Find Radiant Power?

$$I_f = \frac{24\text{V} - 1.2\text{V}}{680\Omega} = 33.5\text{mA}$$

From the given graph in fig 3-73 (b) we see that Radiant power =  $80\text{mW}$ .

⑰  $V_R = 10\text{V}$ ,  $R = 200\text{k}\Omega$

$$I_R = \frac{10\text{V}}{200\text{k}\Omega} = 50\mu\text{A}$$

Assignment # 3

Solution

Q-1:  $Z_2 = 15\Omega$ , At  $50\text{mA}$  find terminal voltage  $V_2 = ?$   
 At  $I_2 = 25\text{mA}$  the voltage  $V_2 = 6.8\text{V}$

$$\Delta I_2 = 50\text{mA} - 25\text{mA} = 25\text{mA}$$

$$\Delta V_2 = \Delta I_2 Z_2 = (25\text{mA})(15\Omega)$$

$$\Delta V_2 = 0.375\text{V}$$

$$V_2 = V_{2T} + \Delta V_2 = 6.8\text{V} + 0.375\text{V}$$

$$V_2 = 7.175\text{V}$$

Q-2:  $V_2 = 6.8\text{V}$  at  $25^\circ\text{C}$  and  $\text{TC} = +0.004/^\circ\text{C}$   
 Find  $V_2$  at  $70^\circ\text{C} = ?$

$$\Delta T = 70^\circ\text{C} - 25^\circ\text{C} = 45^\circ\text{C}$$

$$\Delta V_2 = V_2 \times \text{TC} \times \Delta T$$

$$= (6.8)(0.0004)(45)$$

$$\Delta V_2 = 0.1224 = 122\text{mV}$$

The zener volt. at  $70^\circ\text{C}$  is:

$$V_2 + \Delta V_2 = 6.8\text{V} + 122\text{mV} = 6.922\text{V}$$

Q-3:  $V_{\text{IN}(\text{min})} = ?$   $Z_2 = 20\Omega$ ,  $V_2 = 14\text{V}$  at  $30\text{mA}$ ,  $I_{2K} = 1.5\text{mA}$

~~$$\Delta V_2 = I_{2T} Z_2 - V_{2K}$$~~

~~$$= 28.5\text{mA}$$~~

~~$$\Delta V_2 = \Delta I_2 Z_2$$~~

~~$$= (40\text{mA} - 30\text{mA})(20\Omega)$$~~

~~$$\Delta V_2 = 0.3\text{V}$$~~

~~$$V_{2T} =$$~~


$$\Delta V_2 = (I_{2T} - I_{2K}) Z_2 = (28.5\text{mA})$$

$$= (30 - 1.5) 20\Omega = 28.5 \times 20 = 0.57\text{V}$$

$$V_{\text{OUT}} = V_{2T} - \Delta V_2 = 14\text{V} - 0.57\text{V} = 13.43\text{V}$$

$$V_{\text{IN}(\text{min})} = I_{2K} R + V_{\text{OUT}} = (1.5)(560) + 13.43$$
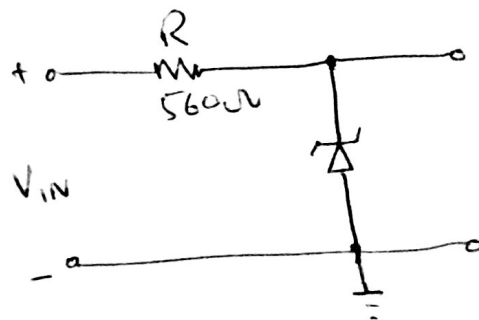
$$V_{\text{IN}(\text{min})} = 14.3\text{V}$$




Q.4.  $V_Z = 5.1V$  at  $I_Z = 49mA$ ,  $I_{ZK} = 1mA$

$Z_Z = 7\Omega$ ,  $I_{ZM} = 70mA$ .

Find  $I_{L(\min)}$  &  $I_{L(\max)}$ ?
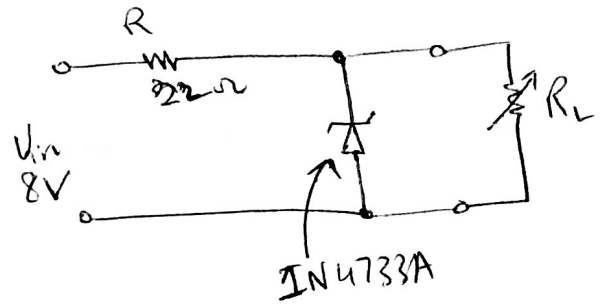
$$\begin{aligned}V_{Z(\min)} &= V_Z - \Delta I_Z Z_Z \\&= 5.1V - (49mA - 1mA)7\Omega \\&= 5.1V - (48mA)(7\Omega) \\&= 5.1V - 0.336 = 4.76V.\end{aligned}$$



$$V_R = 8V - 4.76V = 3.24V$$

$$I_T = \frac{V_R}{R} = \frac{3.24V}{22\Omega} = 147mA$$

$$I_{L(\max)} = I_T - I_{ZK} = \cancel{8V - 4.76V} = 147mA - 1mA$$

$$\boxed{I_{L(\max)} = 146mA}$$

$$\begin{aligned}V_{Z(\max)} &= V_Z + (I_{ZM} - I_Z)(Z_Z) \\&= 5.1V + (70mA - 49mA)(7\Omega) \\&= 5.1V + 0.34V = 5.44V\end{aligned}$$




$$V_R = 8V - 5.44V = 2.56V.$$

$$I_T = \frac{V_R}{R} = \frac{2.56V}{22\Omega} = 116mA$$



$$I_{L(\min)} = I_T - I_{ZM} = 116mA - 70mA$$

$$\boxed{I_{L(\min)} = 46mA.}$$




### Diode Positive Clipping:

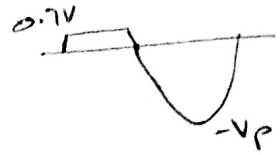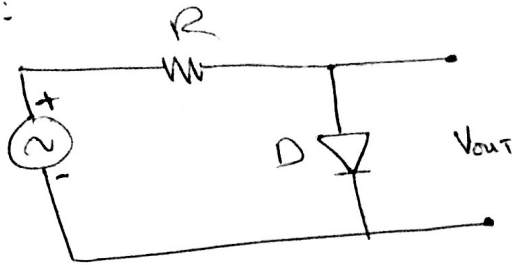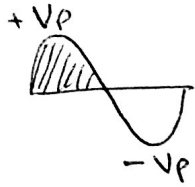




### Diode Negative Clipping:

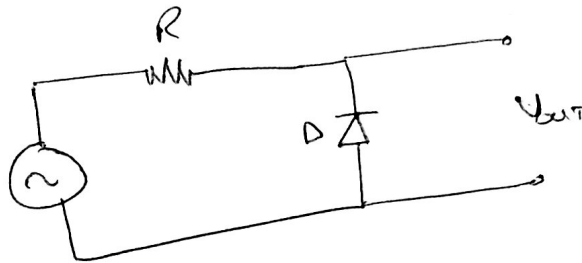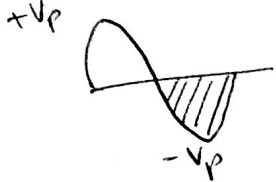

### Positive Bias Diode Clipping:

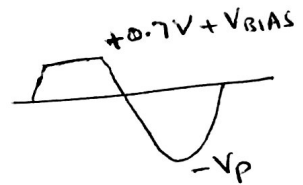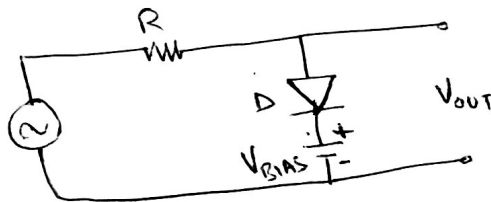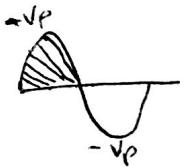

### Negative Bias Diode Clipping:

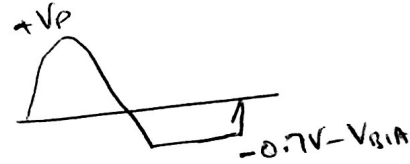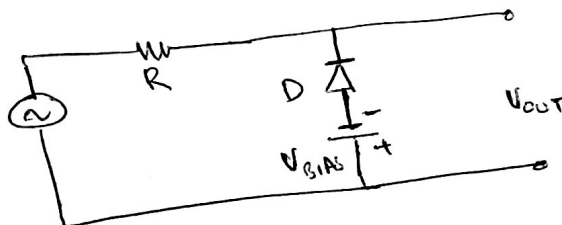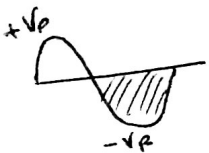

### Zener Limiter:

