

Introduction : characterization of LTI two-port N/w.


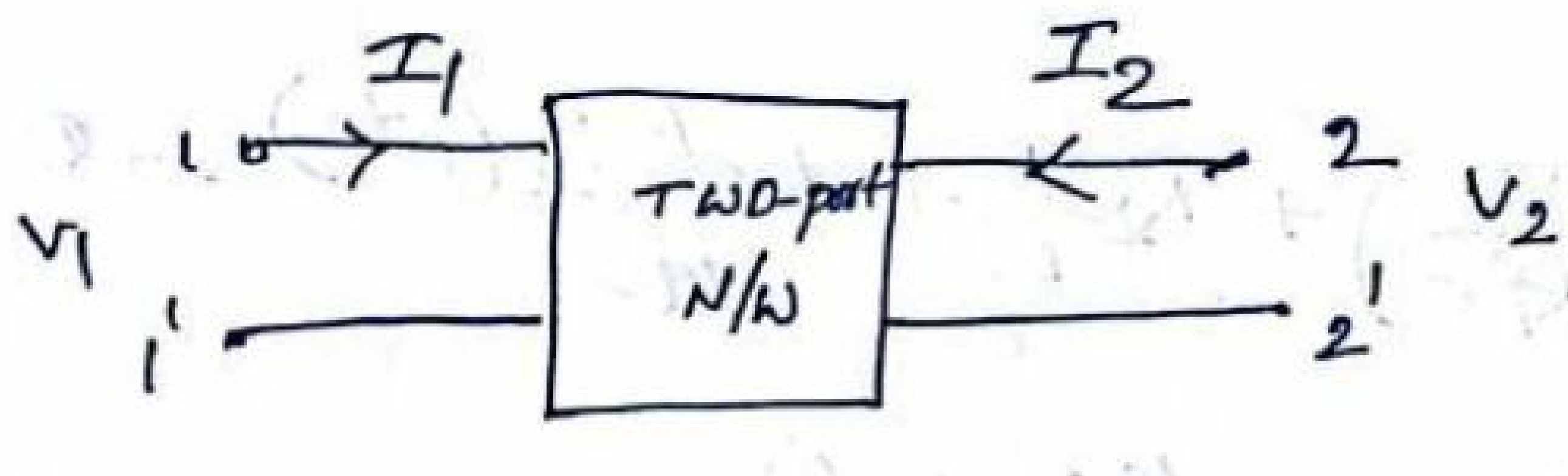


Fig 3-1.

A two-port Network is illustrated in fig. one of ports (labelled 1-1') is called input port 1, while other (labelled 2-2') is termed the output port 2. The external networks that may be connected at input and output ports are called terminations.

Name of parameters.	Express	In terms of
1. open-circuit impedance (Z)	V_1, V_2	I_1, I_2
2. short-ckt admittance (Y)	I_1, I_2	V_1, V_2
3. Transmission (T) or ABCD parameters.	V_1, I_1	V_2, I_2
4. Inverse T	V_2, I_2	V_1, I_1
5. Hybrid (H)	V_1, I_2	I_1, V_2
6. Inverse hybrid (g)	I_1, V_2	V_1, I_2

open circuit Impedance parameter

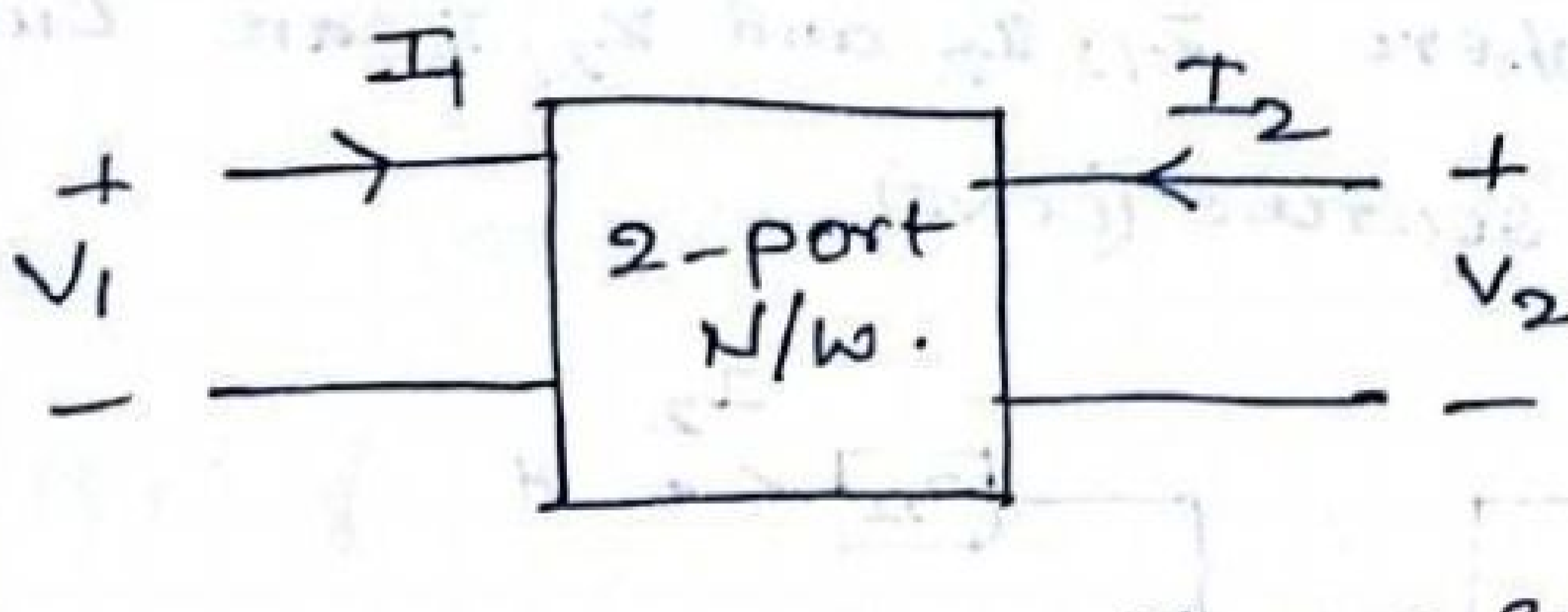

Expressing two-port voltages in terms of two-port currents.

$$\begin{aligned} (V_1, V_2) &= f(I_1, I_2) \\ V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \quad \text{--- (1)}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I]$$

Now, $Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$ i/p impedance with o/p port open-circuited.

$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$ forward transfer impedance with o/p port open-circuited.

$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$ reverse transfer impedance with i/p port open-circuited.

$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$ The o/p impedance with i/p port open-circuited.

$C = \frac{-I_1}{V_2} \Big|_{I_2=0}$ transfer admittance with receiving end open-cted.

$B = \frac{V_1}{-I_2} \Big|_{V_2=0}$ transfer impedance with receiving end short-circuited

$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$ reverse current ratio with receiving end short-circuited.

Condition for reciprocity :-

For network to be reciprocal, Apply V_S at sending end, with receiving end shorted.

$$V_1 = V_S, V_2 = 0, -I_2 = I_2'$$

$$\text{So } V_S = BI_2'$$

$$I_2' / V_S = 1/B \quad \text{--- (4)}$$

Interchange position of excitation & response.

$$V_1 = 0, V_2 = V_S, I_1 = -I_1'$$

Then T-parameter becomes

$$0 = AV_S - BI_2'$$

$$-I_1' = CV_S - DI_2' \quad \text{---}$$

on simplification, $-I_1' = CV_S - \frac{DA}{B}V_S = \frac{(BC-AD)V_S}{B}$

$$\frac{I_1'}{V_S} = \frac{AD-BC}{B} \quad \text{--- (5)}$$

In order to make reciprocal, (4) & (5) should be identical

$$\boxed{AD-BC=1}$$

OR $\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$