

problems

- ① A series RLC circuit has  $R = 250\Omega$ ,  $L = 0.04H$ ,  $C = 0.01\mu F$ . calculate resonant frequency. If a 1-volt source of same frequency as the frequency of resonance is applied to this circuit, calculate the frequencies at which voltage across L and C are maximum. calculate the voltages.

sol/r

Resonant frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.04 \times 0.01 \times 10^{-6}}}$$

$$f_0 = 7960 \text{ Hz}$$

At resonance, the current

$$I_0 = \frac{V}{R} = \frac{1}{25} = 0.04 \text{ A}$$

the frequency at which  $V_L$  is max is

$$f_L = \left(\frac{1}{2\pi}\right) \left[ \frac{1}{\sqrt{LC - \frac{C^2 R^2}{2}}} \right] = 8 \text{ kHz}$$

the frequency at which  $V_C$  is max is

$$f_C = \left(\frac{1}{2\pi}\right) \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} = 7.9 \text{ kHz}$$

The voltage across inductance

$$V_L = I_0 \times L = I_0 \omega_L = 0.04 \times 50 \times 10^3 \times 0.04$$

$$V_L = 80 \text{ V}$$




Voltage across capacitor

$$V_C = I_0 X_C$$

$$= \frac{I_0}{\omega_0 C}$$

$$V_C = \underline{\underline{80V}}$$

## Selectivity and Bandwidth.

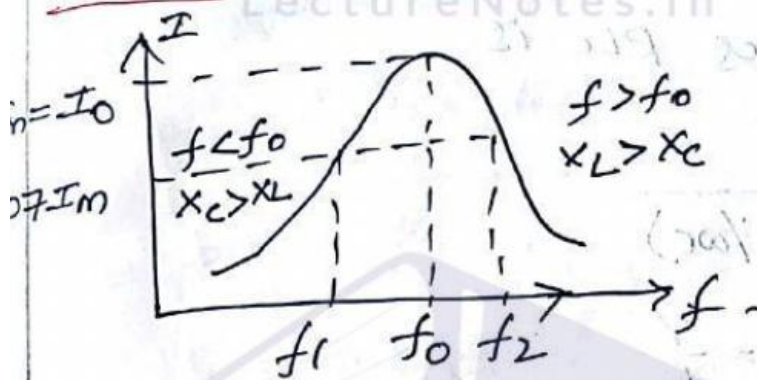

Fig(5) Variation of current in series RLC.

Fig(5) shows the variation of current  $I$  with frequency for smaller values of  $R$ . Thus a series RLC circuit possesses frequency selectivity.

The frequencies  $f_1$  and  $f_2$  at which current  $I$  falls to  $(\frac{1}{\sqrt{2}})$  times its maximum value  $I_0 (=V/R)$  are called half-power frequencies or 3dB-frequencies.

The Bandwidth ( $f_2 - f_1$ ) is called half-power bandwidth or 3dB bandwidth.

$$\boxed{B.W = f_2 - f_1}$$

A resonant circuit is defined

$$\text{selectivity} = \frac{\text{Resonance frequency}}{\text{Bandwidth}} = \frac{f_0}{f_2 - f_1} \quad \text{--- (1)}$$

' $f_1$ ' is lower 3dB frequency or lower half power frequency, and

' $f_2$ ' is higher 3dB freq or upper half-power frequency.

The current in series RLC is

$$I = \frac{V}{R + j(\omega L - 1/\omega C)}$$

At resonance,  $I_0 = \frac{V}{R}$

At upper halfpower freq,  $f_2$

$$|I_2| = \frac{I_0}{\sqrt{2}} = \frac{V}{\sqrt{2}R} = \frac{|V|}{|R + jR|} \quad \text{--- (2)}$$

ie at  $f_2$ ,  $\omega_2 L - \frac{1}{\omega_2 C} = R$

Similarly, at  $f_1$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R$$

Then current at  $f_1$  is given by

$$I_1 = \frac{V}{R - jR} \quad \text{and}$$

$$I_1 = \frac{V}{\sqrt{2}R} = \frac{I_0}{\sqrt{2}} \quad \text{--- (3)}$$