

## Transformer on No load:-

→ A T/R is said to be on no load when the secondary winding is open-circuited.

→ The secondary current is thus zero.

→ When an alternating voltage is applied to the primary, a small current  $I_0$  flows in the primary.


→ The current  $I_0$  is called the no-load current of the transformer.

→ It is made up of two components  $I_m$  and  $I_w$ .

→ The component  $I_m$  is called the magnetizing component.

→ It magnetizes the core. In other words, it sets up a flux in the core and therefore  $I_m$  is in phase with  $\phi_m$ .

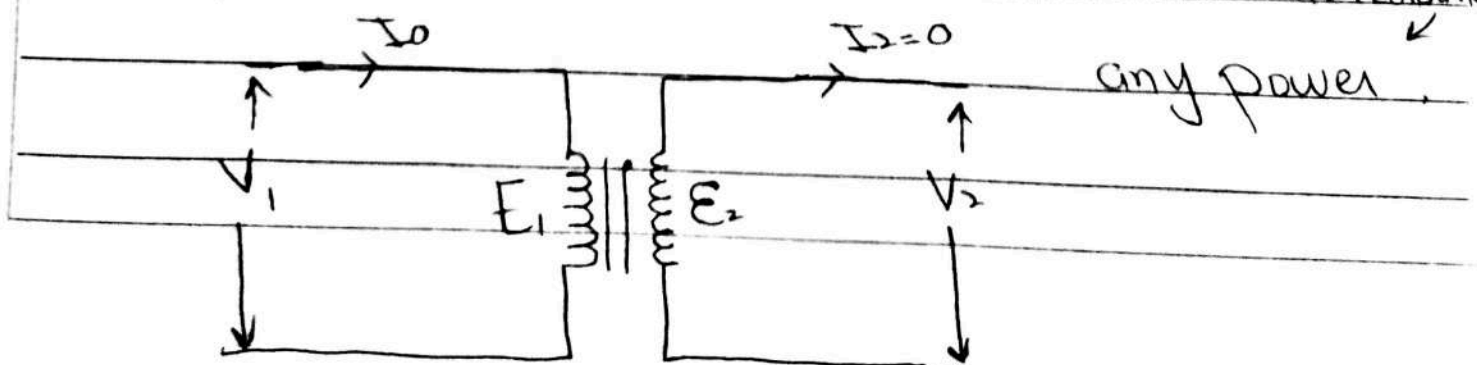→ The current  $I_w$  is also called reactive or wattless component of no-load current as it does not consume



→ The component  $I_w$  supplies the hysteresis and eddy current losses in the core and the negligible  $I^2R$  loss in the primary winding.


→ The current  $I_w$  is called the active component or wattful component of no-load current  $I_0$  and is in phase with the applied voltage  $V_1$ .

→ The no-load current  $I_0$  is small of the order of 3 to 5 percent of the rated current of primary.
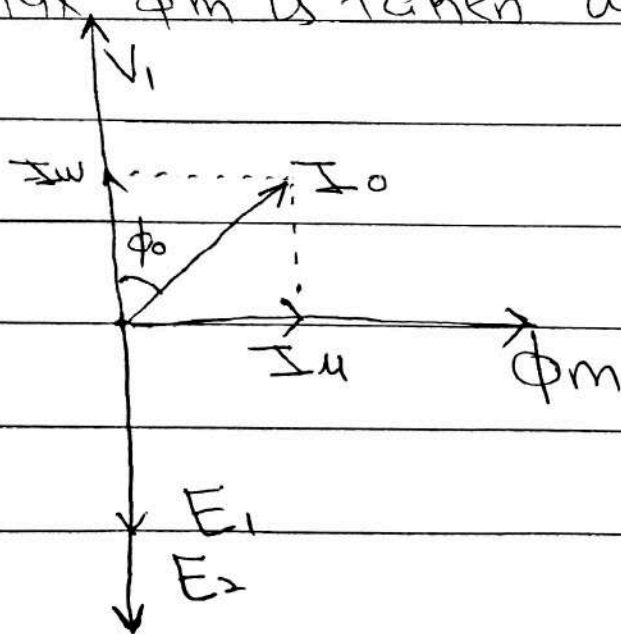
### Phasor Diagram at No load:-

→ An approximate phasor diagram for a TTR under no-load condition is shown below.

→ The flux  $\phi_m$  is taken as the reference phasor.



→ Since  $E_1$  and  $E_2$  are induced by the same flux  $\phi_m$ , hence they will be in phase with each other and other will lag  $\phi_m$  by  $90^\circ$ .

→ If voltage drops in the primary winding are neglected,  $E_1$  will be equal and opposite to the applied voltage  $V_1$ .

→  $I_u$  is in phase with  $\phi_m$  and  $I_w$  is in phase with  $V_1$ .

→ The phasor sum of  $I_u$  and  $I_w$  is  $I_0$ .

→ Angle  $\phi_0$  is called the no-load angle.

From the phasor diagram:

$$I_w = I_0 \cos \phi_0$$

$$I_u = I_0 \sin \phi_0$$

$$I_0 = \sqrt{I_w^2 + I_u^2}$$

Also core loss =  $V_1 I_0 \cos \phi_0 = V_1 I_w$  watts

magnetizing (reactive) Volt Amperes

$$= V_1 I_0 \sin \phi_0 = V_1 I_u \text{ VAR}$$

Also power factor,  $\cos \phi_0 = \frac{I_w}{I_0}$


## Practical Transformer:-

- In an ideal T/R, certain assumptions were made which are not valid in a practical T/R.
- For example, in a practical T/R, the windings have resistance, the core has finite permeability and there is a leakage of flux.
- The efficiency of a practical T/R is not 100 percent due to losses.
- Therefore, in a practical T/R, we shall consider all these imperfections.
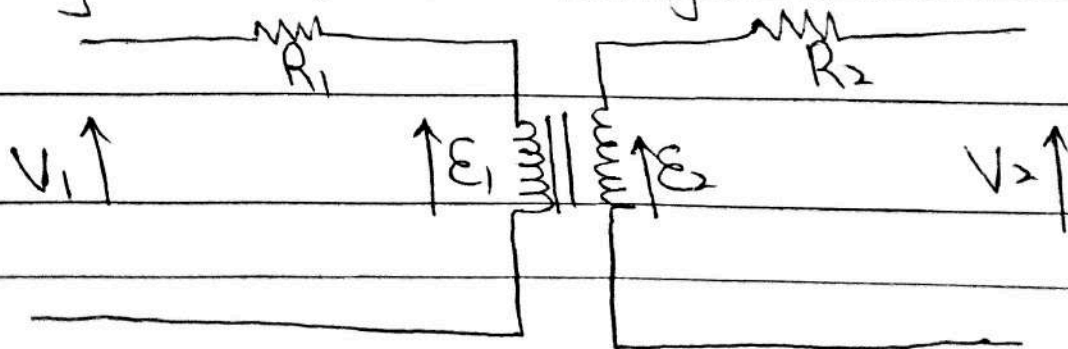
### Winding Resistance:


An ideal T/R is supposed to have no resistance but in actual T/R, there is always some resistance of both primary and secondary windings.

- The effect of resistance is equivalent to an ideal T/R with resistances connected in series with each winding as shown in the figure below:-


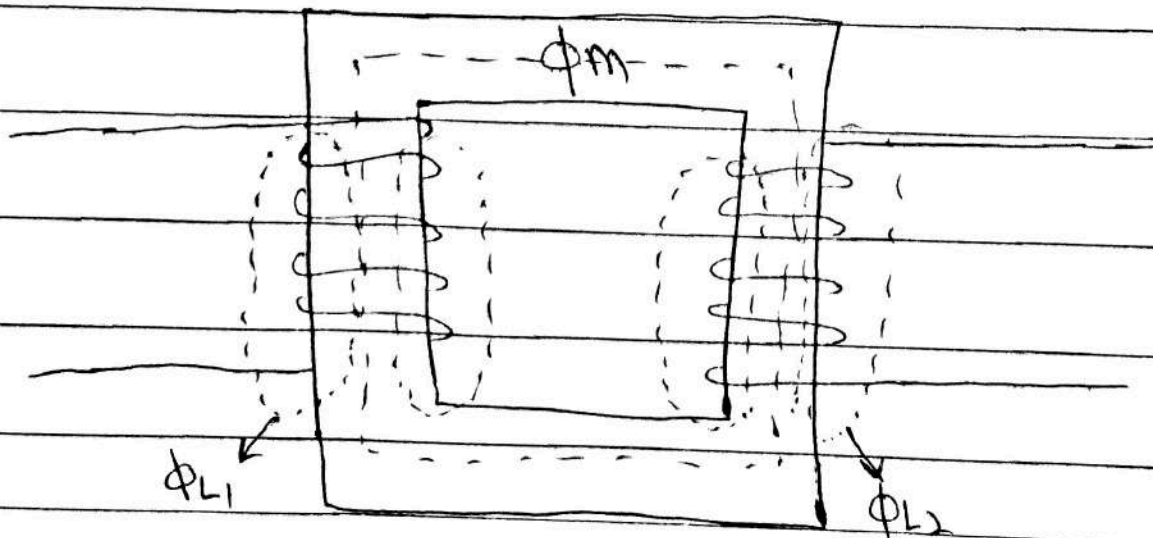
## Leakage Reactance:-

- In an ideal T/R, it was assumed that all the flux produced by the primary winding links both the primary and secondary winding.
- However, in an actual T/R, not all the flux remains within the magnetic core.
- A portion of this flux is diverted to the surrounding air of the winding as the surrounding medium also has some permeability (although it is very much less than that of the core).
- The small portion of the flux, which flows in the surrounding path is known as primary leakage flux denoted by  $\phi_{L1}$  as shown in the fig below.
- The flux  $\phi_{L1}$  links only the primary turns and induces an emf  $E_{L1}$  in the primary winding.



→ Also, the secondary current  $I_2$  produces a flux  $\phi_2$  which opposes the main flux  $\phi_m$ .

→ A portion of this flux is also diverted to the surrounding medium. This leakage flux is called the secondary leakage flux  $\phi_{L2}$ . It only links the secondary turns and induces an emf  $E_{L2}$  in the secondary.

→ Thus, each leakage flux links one winding only and it is caused by the current in that winding alone.


→ The flux which passes completely through the core and links both windings is called mutual flux and is shown as  $\phi_m$ .

→ It should be noted that the induced voltages  $E_{L1}$  and  $E_{L2}$  due to leakage fluxes  $\phi_{L1}$  and  $\phi_{L2}$  are different from induced voltage  $E_1$  and  $E_2$ .

→ As the leakage flux linking with each winding produces a self induced emf in that winding, hence the effect of leakage flux is equivalent to

an inductance in series with each winding such that the voltage drop in each series inductance is equal to that produced by the leakage flux.

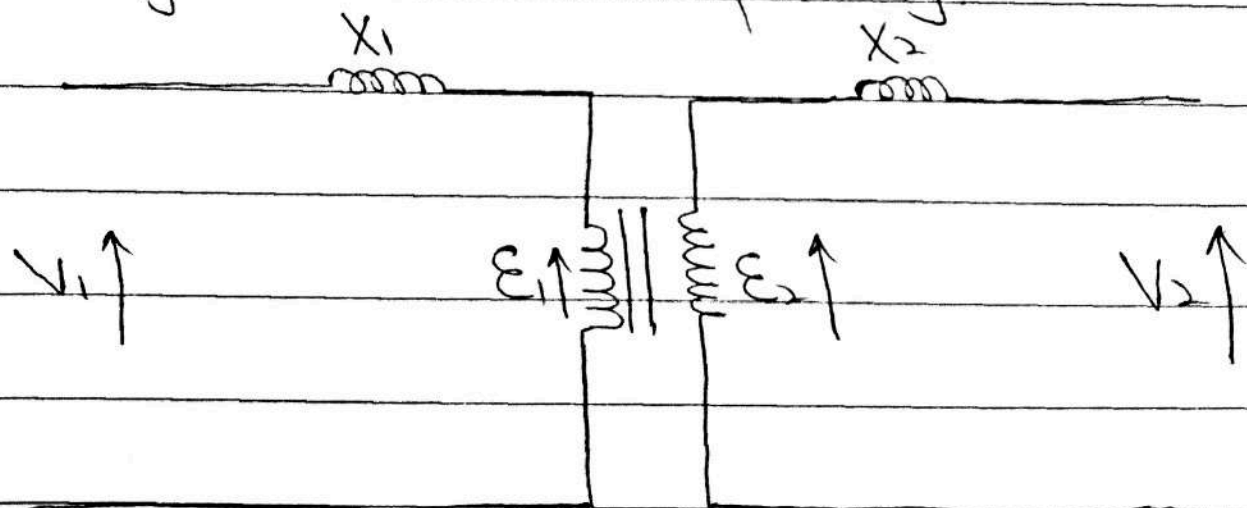→ In other words, a T/R with magnetic flux leakage is equivalent to an ideal T/R with inductive reactance  $X_1$  and  $X_2$  connected in series with the primary and secondary windings respectively, as shown in the below figure. The quantities  $X_1$  and  $X_2$  are known as primary and secondary leakage reactances respectively.



## Transformer on Load:

- As discussed earlier, when the Secondary of the T/R is kept open, it draws the no-load current from the main supply.
- This no-load current  $I_0$  sets up the flux  $\phi_m$  in the core of the T/R.
- Now, when the load is connected to the Secondary of the T/R,  $I_2$  current flows through the secondary winding.
- This Secondary current  $I_2$  sets up the flux  $\phi_2$  in the T/R core.
- This flux  $\phi_2$  opposes the main flux  $\phi_m$  according to Lenz's law.
- As the flux  $\phi_2$  opposes the main flux  $\phi_m$ , the resultant flux of the T/R decreases and this flux reduces the induced emf  $E_1$ . Thus, the strength of  $V_1$  is more than  $E_1$ .
- In order to restore the original value of the main flux in the core, an additional primary current  $I_1'$



is drawn from the main supply.

→ This additional current is used for restoring the original value of the main flux so that  $V_1 = E_1$ . Thus, it is called the primary counterbalancing current.

→ The additional current  $I_1'$  induces  $\mathcal{E}_1$  a flux  $\phi_1'$  so that it cancels the flux  $\phi_2$ .

→ The direction of  $\phi_1'$  is same as that of  $\phi_m$ .

