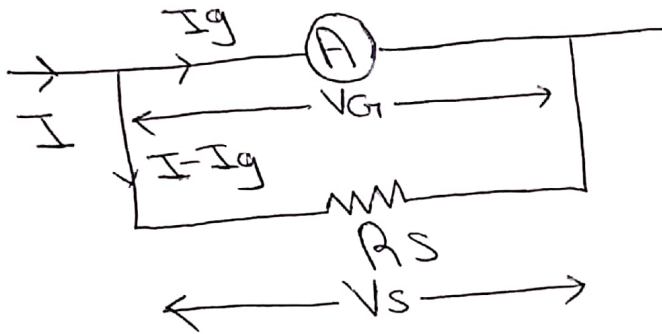


Problem 1:-

A galvanometer gives a F.S.D when the current is 40mA and its resistance is 25Ω . Calculate the value of shunt to be connected in parallel with the meter to enable it to be used as an ammeter for measuring currents upto 50A .



Given Data:-

$$R_G = 25\Omega, I = 50\text{A}$$

$$I_g = 40\text{mA}$$

Required:-

$$R_S = ?$$

Solution:-

$$\text{As } V_G = V_S$$

$$I_g R_G = (I - I_g) R_S$$

$$R_S = \frac{I_g R_G}{I - I_g}$$

$$R_S = \frac{(0.04)(25)}{50 - 0.04}$$

$$\boxed{R_S = 0.02\Omega} \quad \text{Ans:-}$$

Problem 2:-
 A galvanometer gives FSD for a current of 10mA . Neglecting the resistance of the instrument, calculate the appropriate value of series resistance needed to enable the instrument to enable the instrument to measure up to:-

a):- 20V

b):- 100V .


Given Data:-

$$I_g = 10\text{mA}$$

$$V = 20\text{V}$$

neglect G ,

$$\Rightarrow G = 0\Omega$$

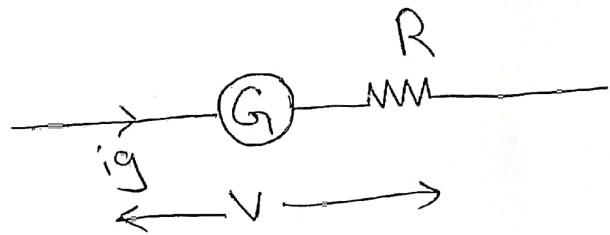

Required :-

$$R = ?$$

Solution:-

$$V = I_g(G + R)$$

$$\frac{V}{I_g} = G + R$$

$$R = \frac{V}{I_g} - G$$

a):- $R = \frac{20}{0.01} - 0$

$$R = 2\text{k}\Omega \text{ Ans:-}$$

b):- $R = \frac{100}{10 \times 10^{-3}} - 0$


$$R = 10\text{k}\Omega \text{ Ans:-}$$

Problem 3:-
 A meter of resistance 50Ω has a f.s.d of 4mA .
 Determine the value of shunt resistance required in
 order that f.s.d should be:-

a) 15mA

b) 20A

Given Data:-

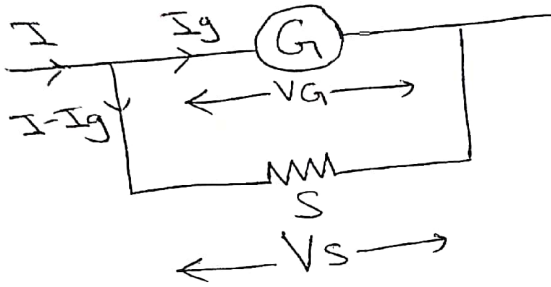

$G = 50\Omega$

$I_g = 4\text{mA}$

Required:-

$S = ?$

b) $I = 20\text{A}$

$$S = \frac{(0.2)}{20 - 0.004}$$

$$S = \frac{0.2}{19.996}$$

Solution :-

$$S = \frac{I_g G}{I - I_g}$$

a) $I = 15\text{mA}$

$$S = \frac{(0.004)(50)}{(0.015) - (0.004)}$$

$S = 0.0105\Omega$ Ans:-

$$S = \frac{0.2}{0.011} \Rightarrow S = 18.18\Omega \text{ Ans:-}$$

Problem 4:-

A moving coil instrument having a resistance of $20\ \Omega$ gives a f.s.d when the current is 5mA . Calculate the value of resistance to be connected in series with the instrument so that it can be used as a voltmeter for measuring p.d upto 200V .

Given Data:-

$$G = 50\ \Omega$$

$$I_g = 5\text{mA}$$

$$V = 200\text{V}$$

Required :-

$$R = ?$$

Solution :-

In order to convert it into voltmeter, we will use:-

$$V = I_g (G + R)$$

$$\frac{V}{I_g} = G + R$$

$$R = \frac{200}{5 \times 10^{-3}} - 50$$

$$R = 40,000 - 50$$

$$\boxed{R = 39.95\ \text{k}\Omega} \quad \text{Ans:-}$$

Problem 5:-

A meter has a resistance of 40Ω and registers a maximum deflection when a current of 15mA flows. Calculate the value of resistance that converts the meter into:-

- a) An ammeter with a maximum deflection of 50A
b) A voltmeter with a range of $0-250\text{V}$.

Given data:-

$$G = 40\Omega$$

$$I_g = 15\text{mA}$$

a) $I = 50\text{A}$

b) $V = 250\text{V}$

Required:-

a) $S = ?$

b) $R = ?$

Solution:-

a) As $R_s = \frac{I_g R_g}{I - I_g} = \frac{(15 \times 10^{-3})(40)}{(50 - 15 \times 10^{-3})} = \frac{0.6}{49.98} = \boxed{0.012 \text{ in parallel}}$
Ans:-

b) $V = I_g (G + R)$
 $R = \frac{V}{I_g} - G = \frac{250}{0.015} - 40 = \boxed{16.62 \text{K}\Omega \text{ in series}}$
Ans:-