


Wattmeter:-

"A wattmeter is an instrument for measuring electrical power in a circuit"

The below fig shows typical connections of a wattmeter used for measuring power supplied to a load. The instrument has two coils.

1) a current coil, which is connected in series with the load like an ammeter. And,

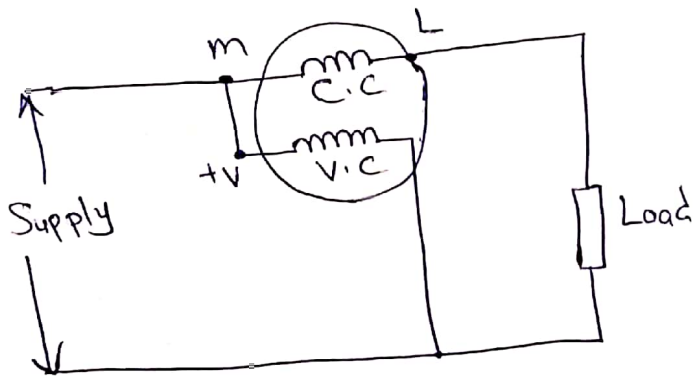
2) a voltage coil, which is connected in parallel with the load, like a voltmeter.



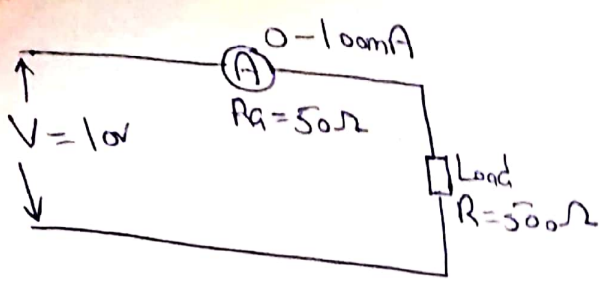Problem:-

An ammeter has a f.s.d of 100mA and a resistance of 50Ω . The ammeter is used to measure the current in a load of resistance 500Ω when the supply voltage is 10V. Calculate:-

- expected ammeter reading.
- The actual current in the ckt.
- The power dissipated in the ammeter
- The power dissipated in the load.



a): expected ammeter reading = $\frac{V}{R+R_a}$

as we are neglecting R_a

$$= \frac{10}{500} = \boxed{20\text{mA}}$$

b): Actual ammeter reading :-

$$= \frac{V}{R+R_a} = \frac{10}{500+50} = \boxed{18.18\text{mA}}$$

c): power dissipated in ammeter :-

$$P_a = I^2 R_a = (18.18 \times 10^{-3})^2 (50)$$

$$\boxed{P_a = 16.53\text{mW}}$$

d): power dissipated in load :-

$$P_L = I^2 R = (18.18 \times 10^{-3})^2 (500) = \boxed{165.3\text{mW}}$$


problem:-

a): A current of 20A flows through a load having a resistance of 2Ω. Determine the power dissipated in the load:

Solⁿ:- power dissipated in the load, $P = I^2 R$

$$= (20)^2 (2) = \boxed{800\text{W}}$$

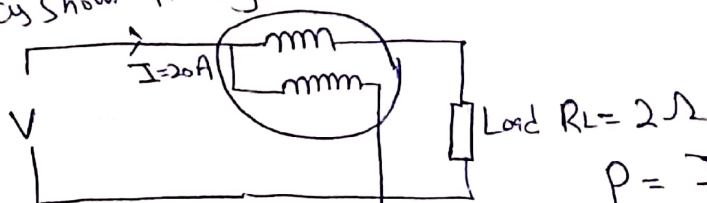b): A wattmeter whose current coil resistance is 0.01Ω is connected as shown in fig below. Determine the wattmeter reading:




$$P = I^2 (R_s + R_L)$$

$$P = (20)^2 (0.01 + 2)$$

$$\boxed{P = 804\text{W}}$$

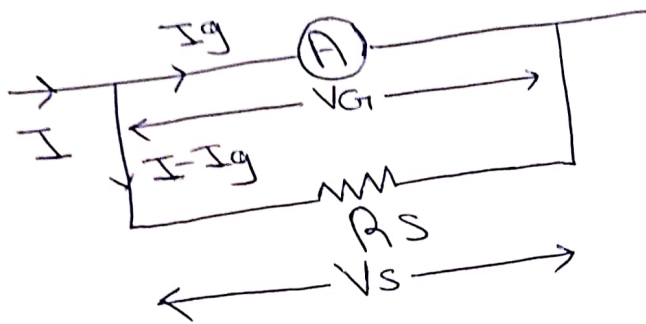Problem 1 :-

A galvanometer gives a F.S.D when the current is 40mA and its resistance is 25Ω . Calculate the value of Shunt to be connected in parallel with the meter to enable it to be used as an ammeter for measuring currents upto 50A .



Given Data :-

$$R_g = 25\Omega, I = 50\text{A}$$

$$I_g = 40\text{mA}$$

Required :-

$$R_s = ?$$

Solution :-

$$\text{As } V_g = V_s$$

$$I_g R_g = (I - I_g) R_s$$

$$R_s = \frac{I_g R_g}{I - I_g}$$

$$R_s = \frac{(0.04)(25)}{50 - 0.04}$$

$$\boxed{R_s = 0.02\Omega} \quad \text{Ans :-}$$

Problem 2:
 A galvanometer gives FSD for a current of 10mA . Neglecting the resistance of the instrument, calculate the appropriate value of series resistance needed to enable the instrument to enable the instrument to measure up to:-

a):- 20V

b):- 100V .


Given Data:-

$I_g = 10\text{mA}$

$V = 20\text{V}$

neglect G

$\Rightarrow G = 0.5\Omega$

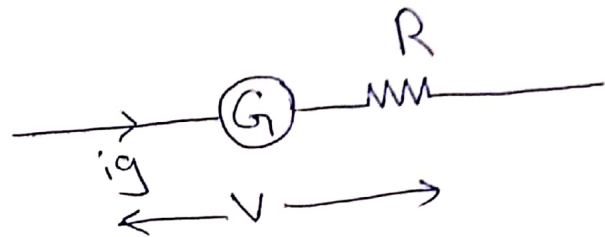

Required :-

$R = ?$

Solution:-

$V = I_g(G + R)$

$\frac{V}{I_g} = G + R$

$R = \frac{V}{I_g} - G$

a):- $R = \frac{20}{0.01} - 0$

$R = 2\text{k}\Omega$ Ans:-

b):- $R = \frac{100}{10 \times 10^{-3}} - 0$

$R = 10\text{k}\Omega$ Ans:-


Problem 3:-

A meter of resistance 50Ω has a f.s.d of 4mA .
 Determine the value of shunt resistance required in order that f.s.d should be :- 3)

a) 15mA

b) 20A

Given Data:-

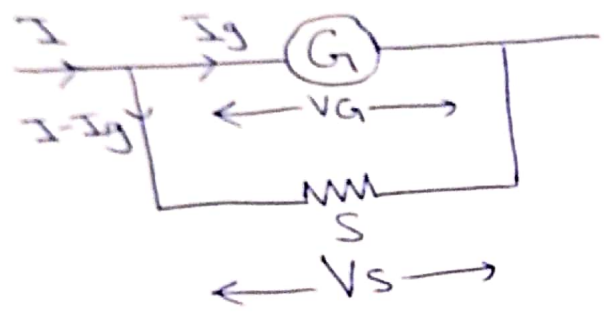

$G = 50\Omega$
 $I_g = 4\text{mA}$

Required:-
 $S = ?$

b) $I = 20\text{A}$

$$S = \frac{(0.2)}{20 - 0.004}$$

$$S = \frac{0.2}{19.996}$$

Solution :-

$$S = \frac{I_g G}{I - I_g}$$

a) $I = 15\text{mA}$

$$S = \frac{(0.004)(50)}{(0.015) - (0.004)}$$

$S = 0.010\Omega$ Ans:-

$$S = \frac{0.2}{0.011} \Rightarrow S = 18.18\Omega \text{ Ans:-}$$

Problem 4:-

A moving coil instrument having a resistance of $20\ \Omega$ gives a f.s.d when the current is 5mA . Calculate the value of resistance to be connected in series with the instrument so that it can be used as a voltmeter for measuring p.d upto 200V .

Given Data:-

$$G = 50\ \Omega$$

$$I_g = 5\text{mA}$$

$$V = 200\text{V}$$

Required :-

$$R = ?$$

Solution :-

In order to convert it into voltmeter, we will use:-

$$V = I_g (G + R)$$

$$\frac{V}{I_g} = G + R$$

$$R = \frac{200}{5 \times 10^{-3}} - 50$$

$$R = 40,000 - 50$$

$$\boxed{R = 39.95\ \text{k}\Omega} \text{ Ans. :-}$$