

Department of Electrical Engineering

Assignment

Date: 26/06/2020

Course Details

Course Title: Electric Power Distribution and Utilization

Module: 4th (B Tech)

Instructor: _____

Total Marks: 50

Student Details

Name: _____

Student ID: _____

Note: Draw neat diagram where necessary. Assume missing details if required.

Q1.	A DC distributor XY, which is 2 wired, 500m long, is fed from both ends at 230V. Various loads of 10 A, 40 A, 30 A and 40 A are tapped at distances of 100m, 250m, 350m and 450 m from the end X respectively. If the area of cross-section of distributor conductor is 2cm^2 , find the minimum consumer voltage. Take the value of resistivity $1.5 \times 10^{-5} \Omega \text{ cm}$	Marks 10
Q2.	A DC distributor AB, which is 2 wired, 3km long, supplies loads of 150A, 200A, 250A and 100A situated 500 m, 1300 m, 2300 m and 3000 m from the supply point A. The resistance of each conductor is 0.02Ω per 1000 m. Calculate the potential difference at each load point if a p.d. of 400 V is maintained at point A.	Marks 10
Q3.	A D.C. distribution system, which is 3-wired, is supplying a load of 7Ω resistance across the positive outer and neutral and a load of 9Ω resistance across negative outer and neutral at the far end of the distributor. The resistance of each conductor is 0.2Ω . If the voltage between any outer and neutral at the load end is to be kept at 260 V, find the voltages at the feeding end.	Marks 10
Q4.	(a) What will happen if the insulating material used for underground cable is hygroscopic and has low dielectric strength?	Marks 05
	(b) Pure rubber cannot be used as an insulating material for underground cable. Justify this statement.	Marks 05
Q5.	(a) In Direct laying method of underground cable, the maintenance cost is high. Justify this statement.	Marks 05
	(b) The Solid system used for laying of underground cable is expensive as compared to direct laid system. Justify this statement.	Marks 05